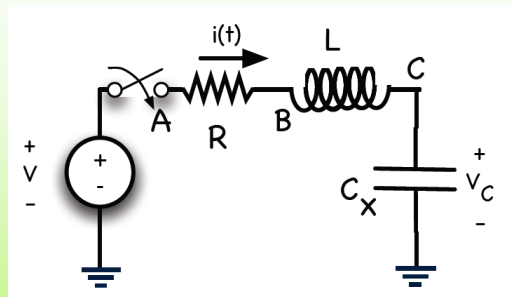



Circuito RLC



$i(t) = 0$ Antes de cortocircuitar

$i(t) \neq 0$ Después de cortocircuitar

Circuito RLC

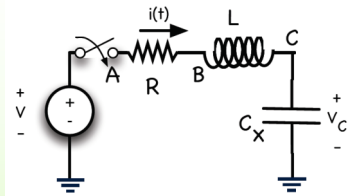

v_A, v_C ? $v_A(t) = u(t)V$

$i_R = i_L = i_C$


$$\begin{cases} \frac{V - v_B}{R} = i_L = i_C = C_X \frac{dv_C}{dt} \\ L \frac{di_L}{dt} = v_B - v_C \end{cases} \Rightarrow \begin{cases} v_B = V - RC_X \frac{dv_C}{dt} \\ v_B = v_C + LC_X \frac{d^2v_C}{dt^2} \end{cases}$$

$$LC_X \frac{d^2v_C}{dt^2} + RC_X \frac{dv_C}{dt} + v_C = V \quad \Leftarrow v_C(t)$$




Circuito RLC

```

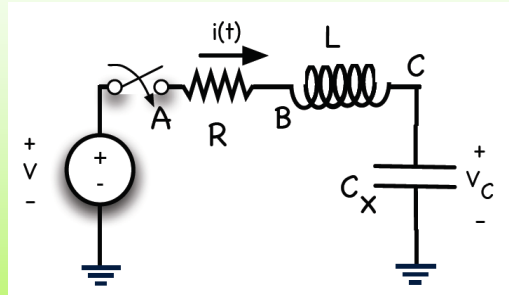CIRCUIT RLC
VX A 0 DC 10
CX C 0 10u
LX B C 1m
RX A B 1K
.IC V(C)=0
.PRINT TRAN V(C)
.TRAN 0.5m 50m UIC
.END
    
```





Resultados de la simulación

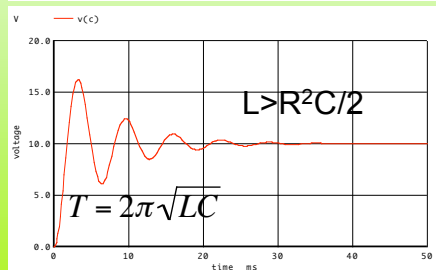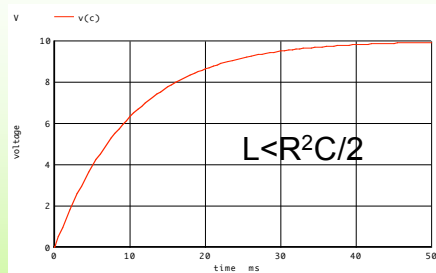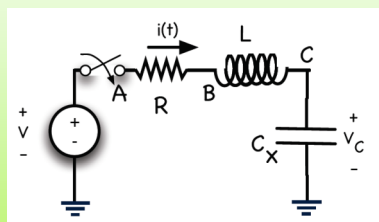

Características temporales

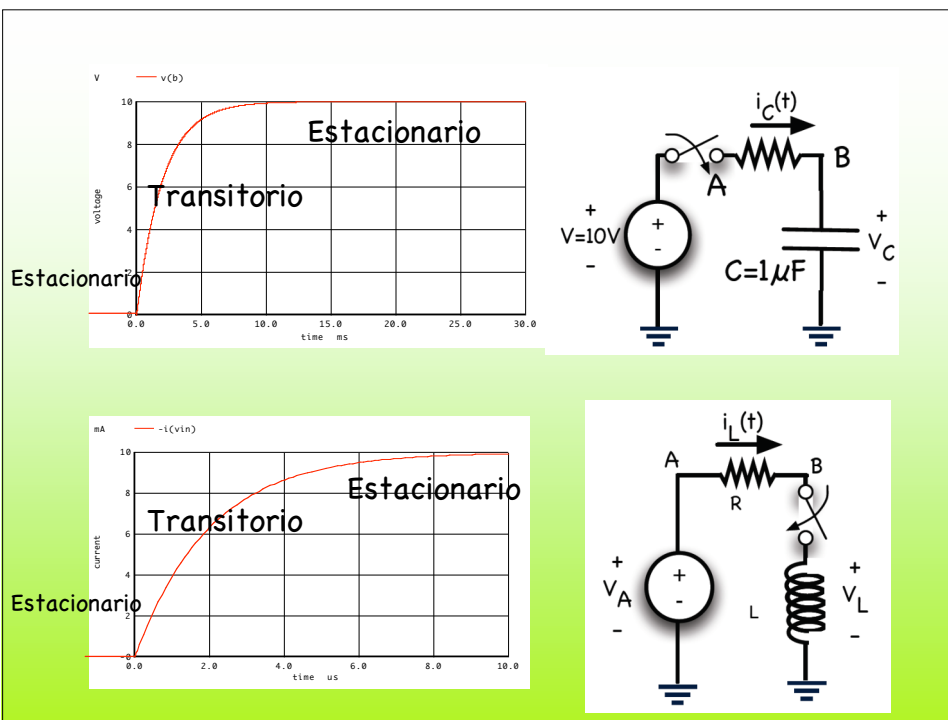- Inicialmente las señales pasan por un período transitorio
- Pasado este período la señal se estabiliza y pasa a un estado estacionario



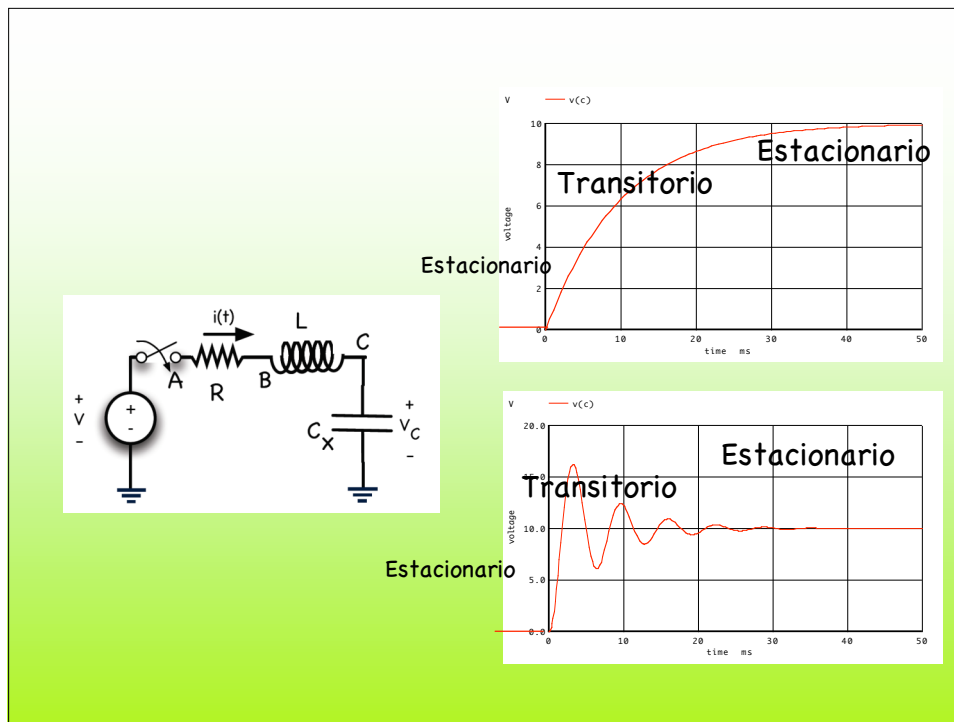

Uso de ecuaciones diferenciales

- Relativamente simple para circuitos RC y RL

$$RC \frac{dV_C(t)}{dt} = V - V_C(t)$$

- Complejo para circuitos con varios componentes (ej. RLC)

$$LC_X \frac{d^2 v_C}{dt^2} + RC_X \frac{dv_C}{dt} + v_C = V$$

- Uso de metodologías de resolución simples: Formulismo de Laplace

La transformada de Laplace

- Simplificación de funciones temporales


$$V(s) = \int_0^{\infty} v(t)e^{-st} dt$$

$$v(t) \xrightarrow{\mathcal{L}} V(s)$$

- Me permitirá usar las mismas técnicas de circuitos usadas hasta ahora

Recall the unit step function $u(t)$ defined by
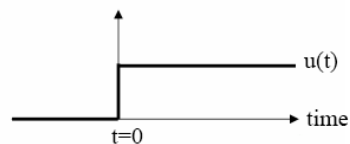
$$u(t) = \begin{cases} 0 & \text{for } t < 0 \text{ s} \\ 1 & \text{for } t \geq 0 \text{ s} \end{cases}$$




Then the Laplace transform of a unit step function is

$$\underline{\underline{\mathcal{L}[u(t)]}} = \int_0^{\infty} u(t)e^{-st} dt = \int_0^{\infty} e^{-st} dt = -\frac{1}{s}e^{-st} \Big|_0^{\infty} = -\frac{1}{s}(0 - 1) = \underline{\underline{\frac{1}{s}}}$$

For the decaying exponential $e^{-at}u(t)$, where $a > 0$, we have that

$$\begin{aligned} \underline{\underline{\mathcal{L}[e^{-at}u(t)]}} &= \int_0^{\infty} e^{-at}u(t)e^{-st} dt = \int_0^{\infty} e^{-(s+a)t} dt \\ &= -\frac{1}{s+a}e^{-(s+a)t} \Big|_0^{\infty} = -\frac{1}{s+a}(0 - 1) = \underline{\underline{\frac{1}{s+a}}} \end{aligned}$$

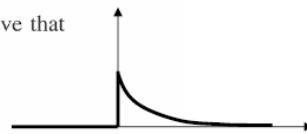

Linealidad de la T.L

$$\mathcal{L}[x(t)] = X(s)$$

$$\mathcal{L}[y(t)] = Y(s)$$

$$\begin{aligned}\mathcal{L}[x(t)k + y(t)r] &= k \mathcal{L}[x(t)] + r \mathcal{L}[y(t)] \\ &= kX(s) + rY(s)\end{aligned}$$

Aplicación de la linealidad:

Let us find the Laplace transform of $f(t) = 3(1 - e^{-2t})u(t)$.

Since we can express this function in the form

$$f(t) = (3 - 3e^{-2t})u(t) = 3u(t) - 3e^{-2t}u(t) = f_1(t) + f_2(t)$$

where $f_1(t) = 3u(t)$ and $f_2(t) = -3e^{-2t}u(t)$. Then by the linearity property of the Laplace transform

$$\begin{aligned}\mathcal{L}[f(t)] &= \mathcal{L}[3u(t)] + \mathcal{L}[-3e^{-2t}u(t)] = 3\mathcal{L}[u(t)] - 3\mathcal{L}[e^{-2t}u(t)] \\ &= 3\left(\frac{1}{s}\right) - 3\left(\frac{1}{s+2}\right) = \frac{3(s+2) - 3s}{s(s+2)} = \frac{6}{s(s+2)}\end{aligned}$$

Problema propuesto 3.2

- Aplicando la propiedad de linealidad. Calcular la transformada de Laplace de:

$$y(t) = 2(e^{-4t} - e^{-3t})u(t)$$

$$\mathcal{L}[y(t)] = Y(s) = ?$$

$$\text{Ayuda: } \mathcal{L}[u(t)e^{at}] = 1/(s-a)$$

Tabla de Transformadas

$f(t)$	Property	$F(s)$
$f(t)$	Definition	$\int_0^\infty f(t)e^{-st} dt$
$f_1(t) + f_2(t)$	Linearity	$F_1(s) + F_2(s)$
$Kf(t)$	Linearity	$KF(s)$
★ $\frac{df(t)}{dt}$	Differentiation	$sF(s) - f(0)$
★ $\frac{d^2f(t)}{dt^2}$	Differentiation	$s^2F(s) - sf(0) - \frac{df(0)}{dt}$
$\int_0^t f(t) dt$	Integration	$\frac{1}{s}F(s)$
$tf(t)$	Complex differentiation	$-\frac{dF(s)}{ds}$
$e^{-at}f(t)$	Complex translation	$F(s + a)$
$f(t - a)u(t - a)$	Real translation	$e^{-as}F(s)$

Note that the Laplace transform is related to the "initial conditions".

Tabla de Transformadas

$f(t)$	$L\{f(t)\}$	$f(t)$	$L\{f(t)\}$
$\delta(t)$	1	$u(t)$	$\frac{1}{s}; s > 0$
e^{at}	$\frac{1}{s-a}; s > a$	t	$\frac{1}{s^2}; s > 0$
$\sin(at)$	$\frac{a}{s^2 + a^2}; s > 0$	$\cos(at)$	$\frac{s}{s^2 + a^2}; s > 0$
$t^n e^{at}$	$\frac{n!}{(s-a)^{n+1}}; s > a$	$e^{at} \sin(kt)$	$\frac{k}{(s-a)^2 + k^2}; s > a$
$e^{at} \cos(kt)$	$\frac{s-a}{(s-a)^2 + k^2}; s > a$	$t^n; n = \{1, 2, \dots\}$	$\frac{n!}{s^{n+1}}; s > 0$
$2 K e^{at} \cos(\beta t + \arg K)$	$\frac{K}{s-\alpha-j\beta} + \frac{K^*}{s-\alpha+j\beta}$		
$cf(t)$	$cF(s)$		
$f_1(t) + f_2(t)$	$F_1(s) + F_2(s)$		
$f'(t)$	$sF(s) - f(0)$		
$f^{(n)}(t)$	$s^n F(s) - s^{n-1}f(0) - \dots - f^{(n-1)}(0)$		
$t^n f(t)$	$(-1)^n F^{(n)}(s)$		
$e^{at} f(t)$	$F(s-a)$		
$\delta(t-a)$	e^{-as}		

Ventajas de la T.L.

- Las ecuaciones diferenciales se convierten en ecuaciones algebraicas

$$RC \frac{dV_C(t)}{dt} = V - V_C(t)$$

$$V_C(0) = \frac{dV_C(0)}{dt} = 0 \quad (\text{Condiciones iniciales})$$

↓

$$RC[sV_C(s) - V_C(0)] = \frac{V}{s} - V_C(s)$$

$$V_C(s) = \frac{V}{s(1 + sRC)} \xrightarrow{\mathcal{L}^{-1}} V_C(t) = V \left(1 - e^{-\frac{t}{RC}} \right) u(t)$$

