
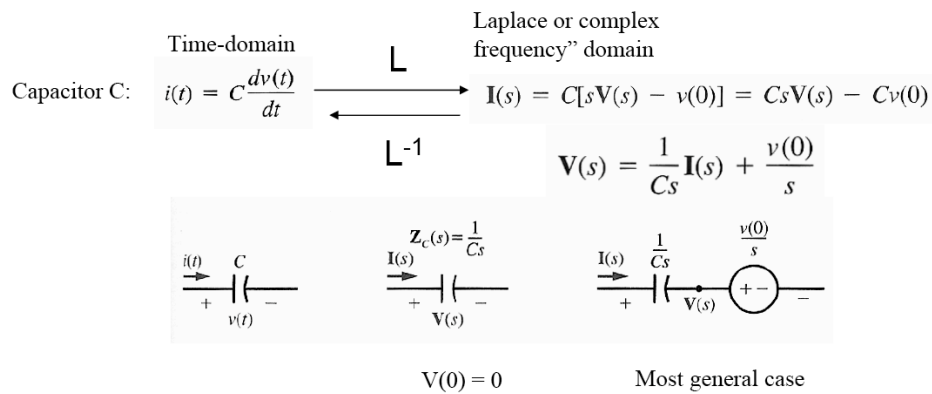


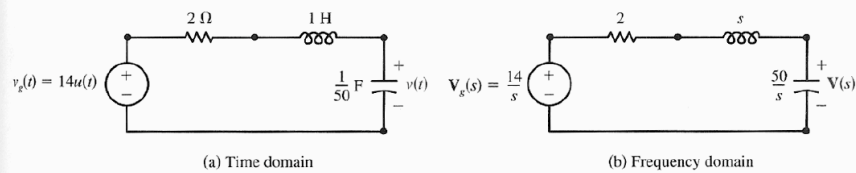

Suppose that the series RLC circuit shown in Fig. 5.40a has zero initial conditions. Let us find the step response $v(t)$.



$$\longrightarrow \mathbf{V}(s) = \frac{50/s}{50/s + s + 2} \mathbf{V}_g(s) = \frac{50}{s^2 + 2s + 50} \left(\frac{14}{s} \right)$$

$$\mathbf{V}(s) = \frac{700}{s(s^2 + 2s + 50)} = \frac{K_1}{s} + \frac{K_2}{s + 1 - 7j} + \frac{K_3}{s + 1 + 7j}$$



$$K_1 = \frac{700}{50} = 14 \quad K_2 = \frac{700}{s(s + 1 + 7j)} \Big|_{s = -1 + 7j} = -7 + j$$

$$K_3 = \frac{700}{s(s + 1 - 7j)} \Big|_{s = -1 - 7j} = -7 - j = K_2^*$$


$$V(t) = 14 + 2|K_2|e^{-t} \cos(7t + \arg(K_2))$$

$$V(t) = 14 + 10\sqrt{2}e^{-t} \cos(7t + 3)$$

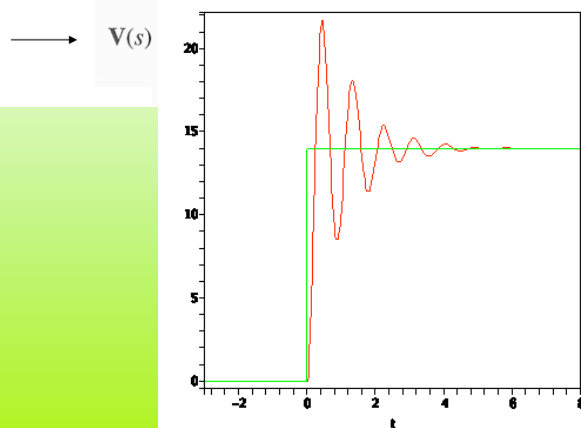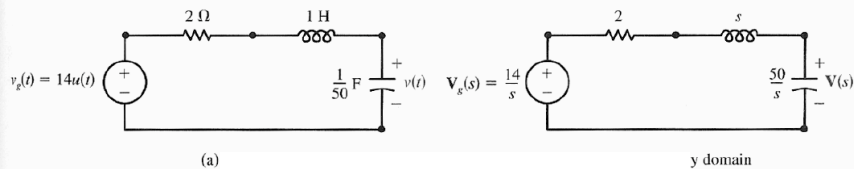Suppose that the series RLC circuit shown in Fig. 5.40a has zero initial conditions. Let us find the step response $v(t)$.



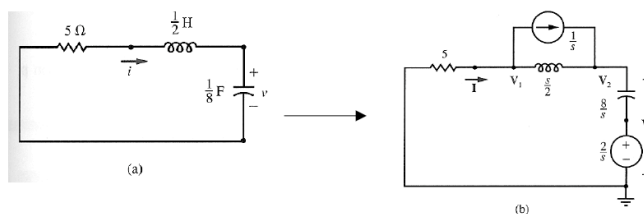Suppose that we wish to find $v(t)$ for the series RLC circuit shown in Fig. 5.41a subject to the initial conditions $v(0) = 2$ V and $i(0) = 1$ A.



$$\frac{V_1}{5} + \frac{V_1 - V_2}{s/2} + \frac{1}{s} = 0 \Rightarrow (s + 10)V_1 - 10V_2 = -5$$



$$\frac{V_2 - V_1}{s/2} + \frac{V_2 - 2/s}{8/s} = \frac{1}{s} \Rightarrow \text{Solve } V_2. \text{ Let } V_2 = V$$

$$-16V_1 + (s^2 + 16)V_2 = 2s + 8$$


$$V_2 = \frac{\begin{vmatrix} s+10 & -5 \\ -16 & 2s+8 \end{vmatrix}}{\begin{vmatrix} s+10 & -10 \\ -16 & s^2+16 \end{vmatrix}} \rightarrow v(t) = 4e^{-2t}u(t) - 2e^{-8t}u(t) = (4e^{-2t} - 2e^{-8t})u(t) \text{ V}$$

$$= \frac{(s+10)(2s+8) - 80}{(s+10)(s^2+16) - 160} = \frac{4}{s+2} + \frac{-2}{s+8}$$

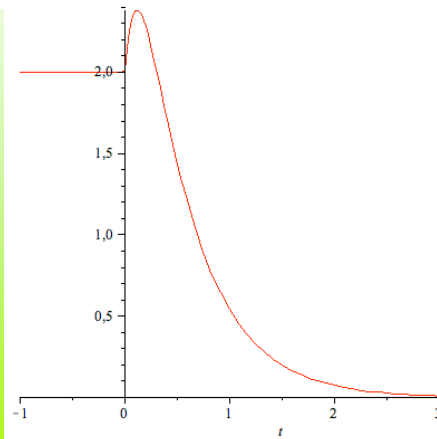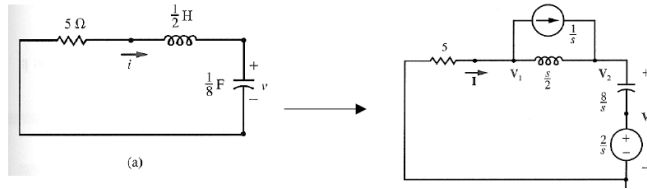Suppose that we wish to find $v(t)$ for the series RLC circuit shown in Fig. 5.41a subject to the initial conditions $v(0) = 2$ V and $i(0) = 1$ A.



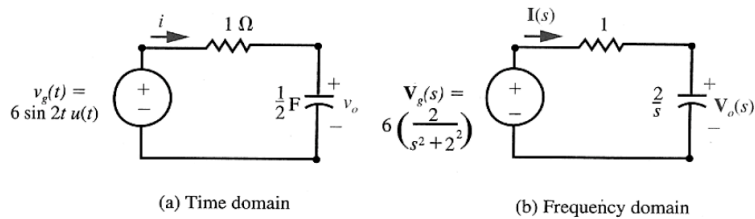Let us determine the responses $i(t)$ and $v_o(t)$ to a sinusoidal excitation (which begins at time $t = 0$ s) for the circuit shown in Fig. 5.42a. The frequency-domain representation of this circuit is shown in Fig. 5.42b.



$$\mathbf{V}_g = 1\mathbf{I} + \frac{2}{s}\mathbf{I} = \frac{s+2}{s}\mathbf{I} \quad \Rightarrow \quad \mathbf{I} = \frac{s}{s+2}\mathbf{V}_g = \frac{12s}{(s+2)(s^2+4)}$$

$$I = \frac{K_1}{s+2} + \frac{K_2}{s-2j} + \frac{K_3}{s+2j}$$

$$K_1 = \left. \frac{12s}{s^2+4} \right|_{s=-2} = -3$$

$$K_2 = \left. \frac{12s}{(s+2)(s+2j)} \right|_{s=2j} = \frac{3}{2} - \frac{3}{2}j \Rightarrow \frac{3\sqrt{2}}{2} \angle -\pi/4$$

$$K_3 = K_2^*$$

$$i(t) = -3e^{-2t} + 3\sqrt{2}\cos(2t - \pi/4)$$

Next to find $v_o(t)$

$$\mathbf{V}_o = \mathbf{Z}_C \mathbf{I} = \frac{2}{s} \frac{12s}{(s+2)(s^2+4)} = \frac{24}{(s+2)(s^2+4)}$$



$$V_o = \frac{K_1}{s+2} + \frac{K_2}{s-2j} + \frac{K_3}{s+2j}$$



$$K_1 = \left. \frac{24}{s^2+4} \right|_{s=-2} = 3$$

$$K_2 = \left. \frac{24}{(s+2)(s+2j)} \right|_{s=2j} = -\frac{3}{2} - \frac{3}{2}j \Rightarrow \frac{3\sqrt{2}}{2} \angle -3\pi/4$$

$$K_3 = K_2^*$$

$$v_o(t) = 3e^{-2t} + 3\sqrt{2} \cos(2t - 3\pi/4)$$

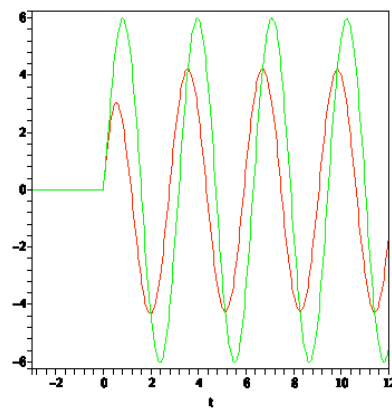
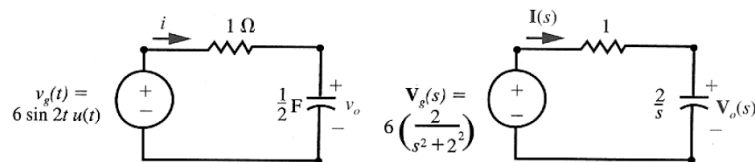
Let us determine the responses $i(t)$ and $v_o(t)$ to a sinusoidal excitation (which begins at time $t = 0$ s) for the circuit shown in Fig. 5.42a. The frequency-domain representation of this circuit is shown in Fig. 5.42b.



Ejemplo

- Obtener $v(t)$

Inicialmente $v(0)=3V$

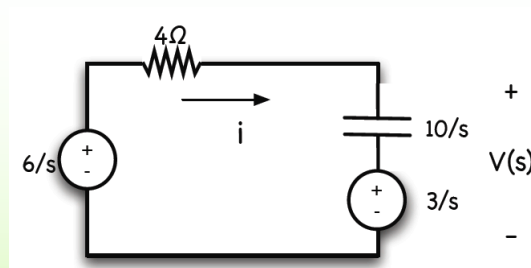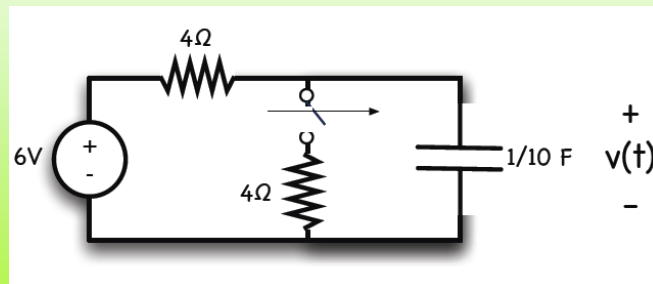

$$i = \frac{3/s}{4 + 10/s}$$

$$V(s) = \frac{3}{s} + i \frac{10}{s} = \frac{6}{s} - \frac{3}{s + 10/4}$$

$$v(t) = (6 - 3e^{-5t/2}) \text{ (para } t > 0)$$

