
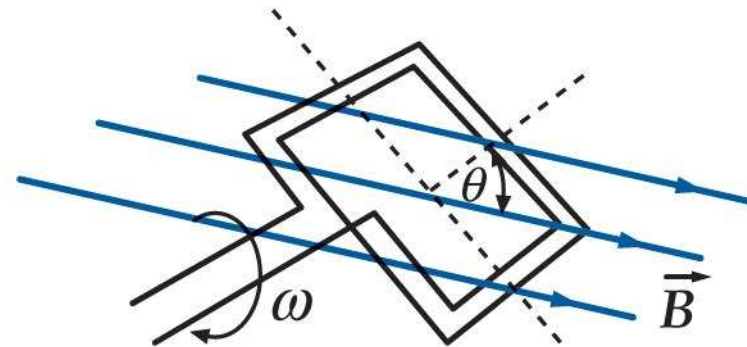


Circuits AC


Generadors de corrent altern

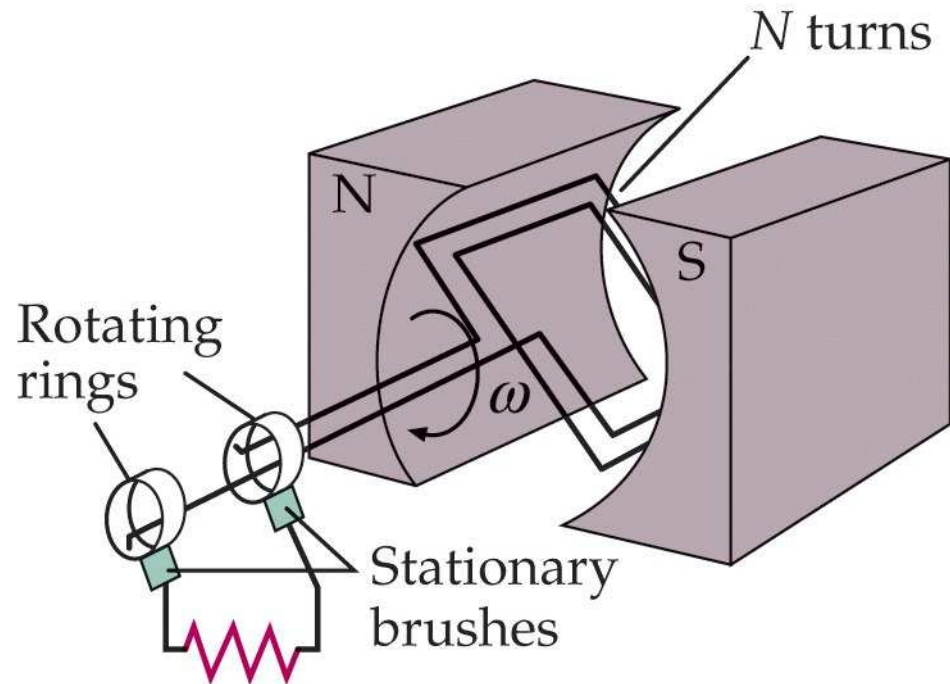


$$\phi_m = NBA \cos \theta = NBA \cos(\omega t + \delta)$$

$$\omega = 2\pi\nu = \frac{2\pi}{T}$$
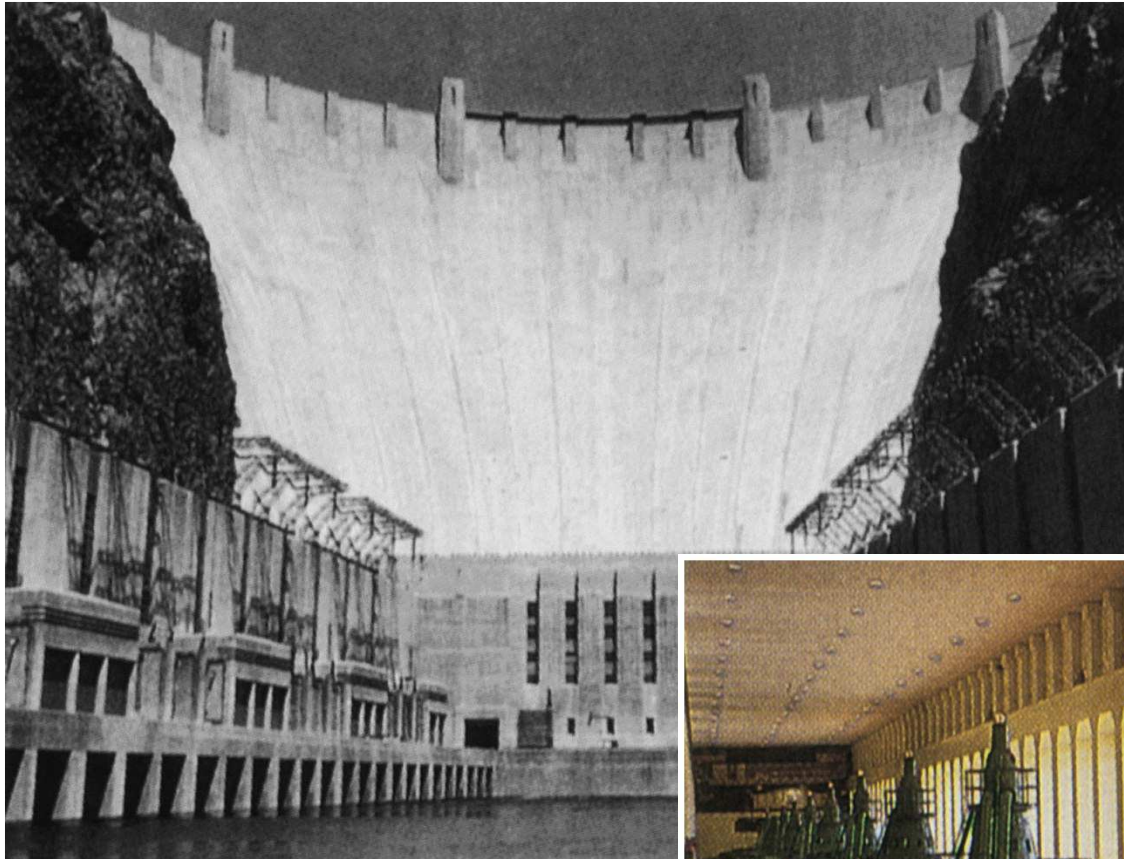
$$\mathcal{E} = -\frac{d\phi_m}{dt} = NBA\omega \sin(\omega t + \delta) = \mathcal{E}_{\max} \sin(\omega t + \delta)$$



Resistències en corrent altern

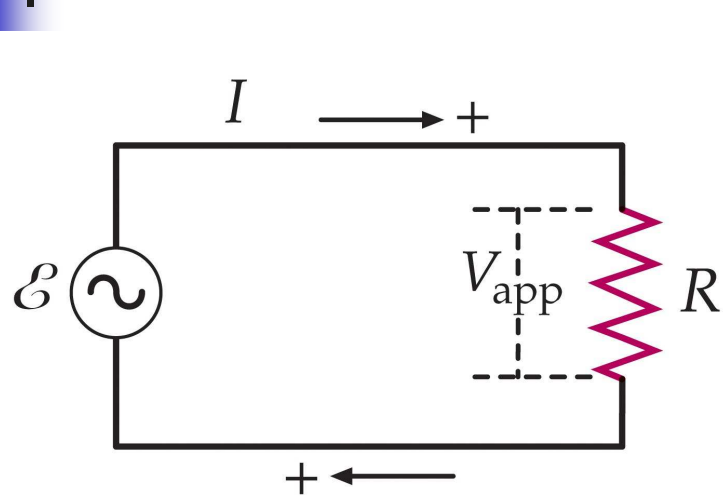



$$V_R = \mathcal{E} = \mathcal{E}_{\text{max}} \sin(\omega t + \delta) \quad \nearrow \frac{\pi}{2}$$

$$= V_{R,\text{max}} \cos \omega t$$

$$I_R = \frac{V_R}{R} = \frac{V_{R,\text{max}}}{R} \cos \omega t = I_{\text{max}} \cos \omega t$$



**Intensitat i potencial
en fase**

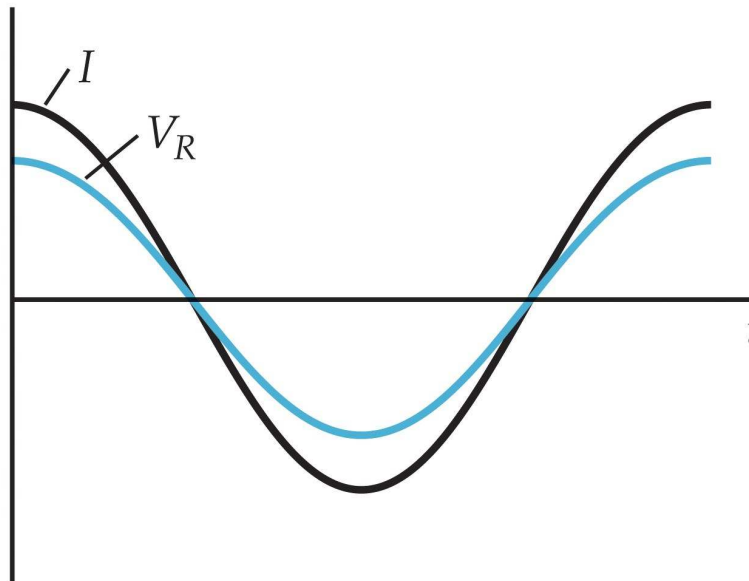

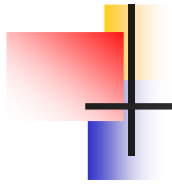

Potència
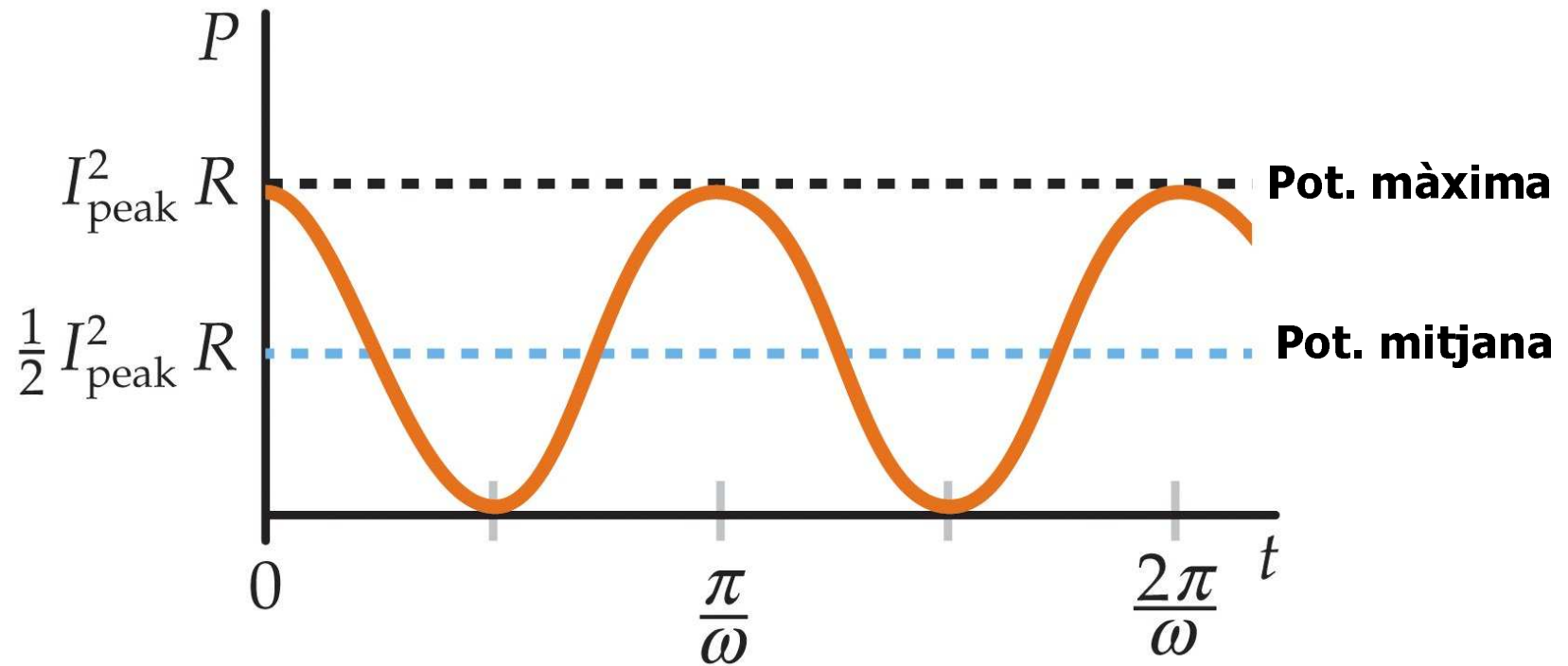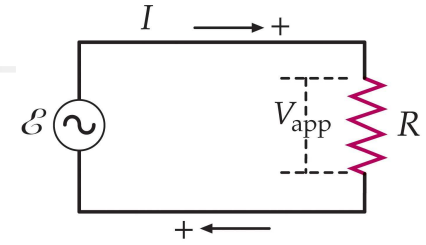
$$P = RI^2 = I_{\max}^2 R \cos^2 \omega t$$
$$= P_{\max} \cos^2 \omega t$$





Valors eficaços

$$I_{\text{ef}} \equiv \sqrt{(I^2)_m}$$

Valor mitjà

senyal sinusoidal


$$(I^2)_m = [(I_{\text{max}} \cos \omega t)^2]_m = \frac{I_{\text{max}}^2}{2}$$

$$I_{\text{ef}} = \frac{I_{\text{max}}}{\sqrt{2}} = 0.707 I_{\text{max}}$$


$$P = I_{\text{max}}^2 R \cos^2 \omega t \quad \longrightarrow \quad P_m = \frac{I_{\text{max}}^2 R}{2} = I_{\text{ef}}^2 R$$

$$P_m = \mathcal{E}_{\text{max}} I_{\text{max}} (\cos^2 \omega t)_m = \frac{1}{2} \mathcal{E}_{\text{max}} I_{\text{max}}$$
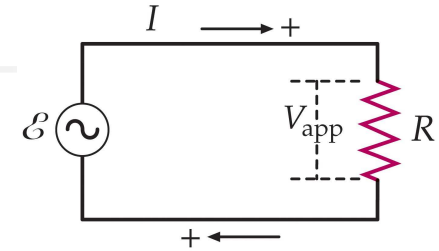
$$P_m = \mathcal{E}_{\text{ef}} I_{\text{ef}}$$



senyal NO sinusoidal

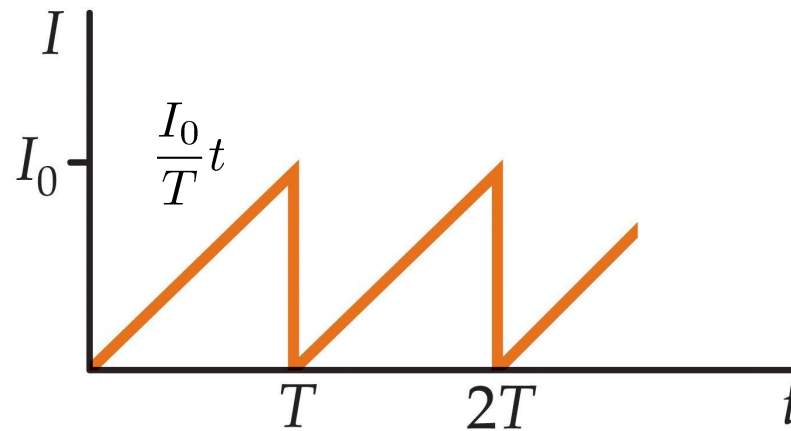


$$I_m = \frac{1}{T} \int_0^T \frac{I_0}{T} t dt = \frac{I_0}{2}$$

$$(I^2)_m = \frac{1}{T} \int_0^T \frac{I_0^2}{T^2} t^2 dt = \frac{I_0^2}{3}$$


$$I_{\text{ef}} \equiv \sqrt{(I^2)_m} = \frac{I_0}{\sqrt{3}}$$

$$P_m = RI_{\text{ef}}^2$$


Bobines en corrent altern

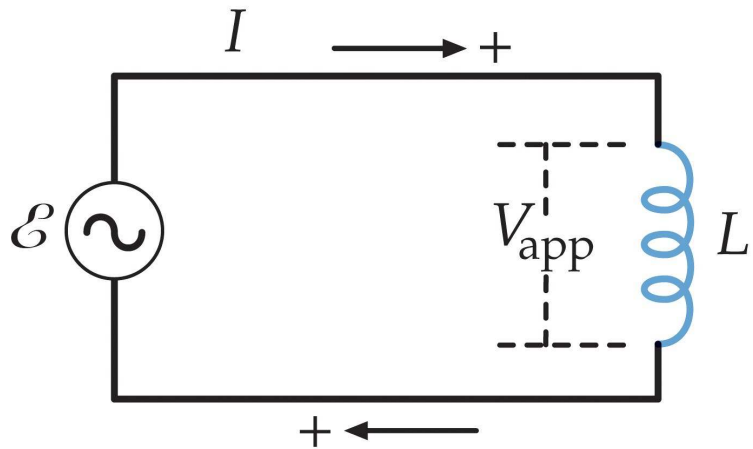

$$V_L = L \frac{dI}{dt}$$

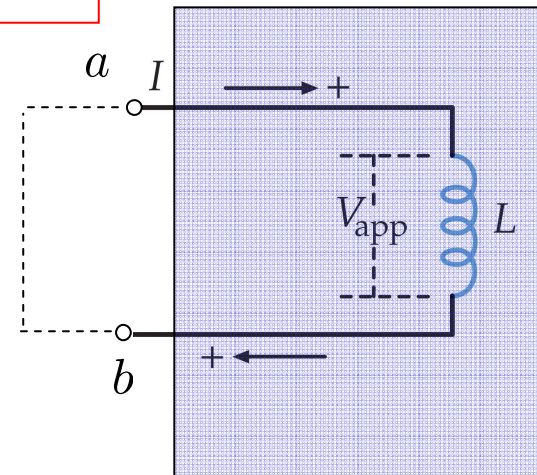

$$\left. \begin{aligned} \oint_C \vec{E} \cdot d\vec{\ell} &= -L \frac{dI}{dt} \\ \oint_C \vec{E} \cdot d\vec{\ell} &= \underbrace{\int_a^b \vec{E} \cdot d\vec{\ell}}_{\substack{\text{Bobina} \\ = 0 \\ \text{Fils conductors ideals}}} + \underbrace{\int_b^a \vec{E} \cdot d\vec{\ell}}_{\substack{\text{Fora} \\ \text{No hi ha camps magnètics variables} \\ \text{Es pot definir el potencial elèctric}}} = V_b - V_a \end{aligned} \right\} V_a - V_b = L \frac{dI}{dt}$$

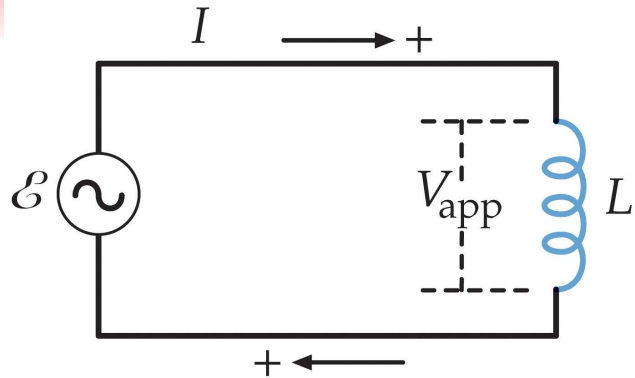


$$V_L = \mathcal{E} = V_{L,\max} \cos \omega t$$

$$V_L = L \frac{dI}{dt} \quad \longrightarrow \quad I = \underbrace{\frac{V_{L,\max}}{\omega L}}_{I_{\max}} \sin \omega t$$

$$I = I_{\max} \cos(\omega t - \pi/2)$$


Desfassament
Potencial adelantat


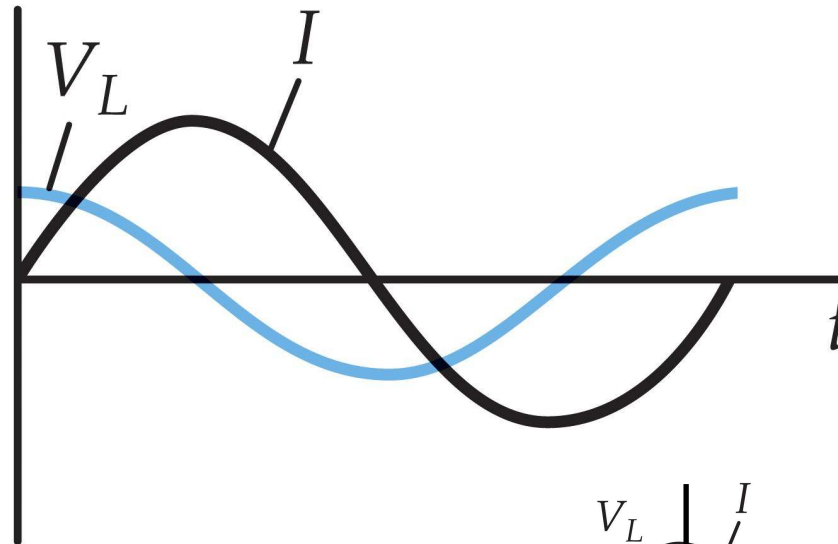


Equivalentment

$$I = I_{\max} \cos(\omega t)$$
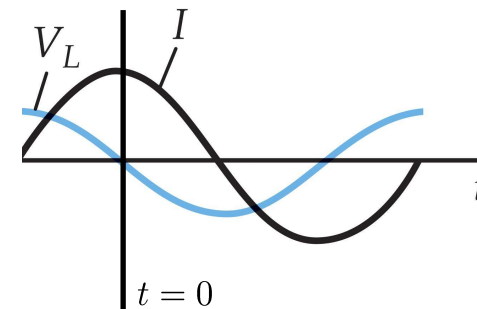
$$V_L = V_{L,\max} \cos(\omega t + \pi/2)$$



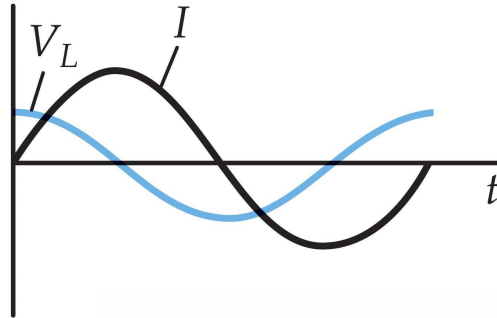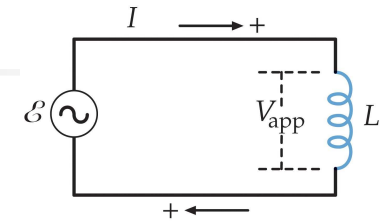

$$I = \frac{V_{L,\max}}{\omega L} \sin \omega t$$


$$I_{\max} = \frac{V_{L,\max}}{\omega L} = \frac{V_{L,\max}}{X_L}$$

$$X_L = \omega L$$


29-24

DEFINITION—INDUCTIVE REACTANCE

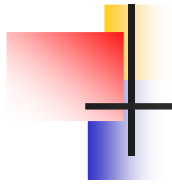També $I_{\text{ef}} = \frac{V_{L,\text{ef}}}{X_L}$




Potència

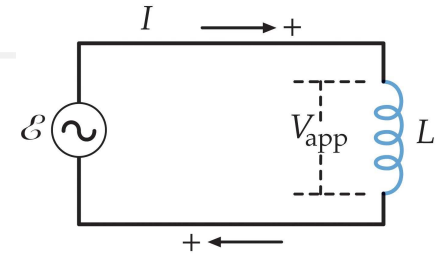

$$P \equiv V_L I = V_{L,\max} I_{\max} \underbrace{\cos \omega t \sin \omega t}_{\frac{1}{2} \sin 2\omega t}$$

$$P_m = 0$$



Condensadors en corrent altern

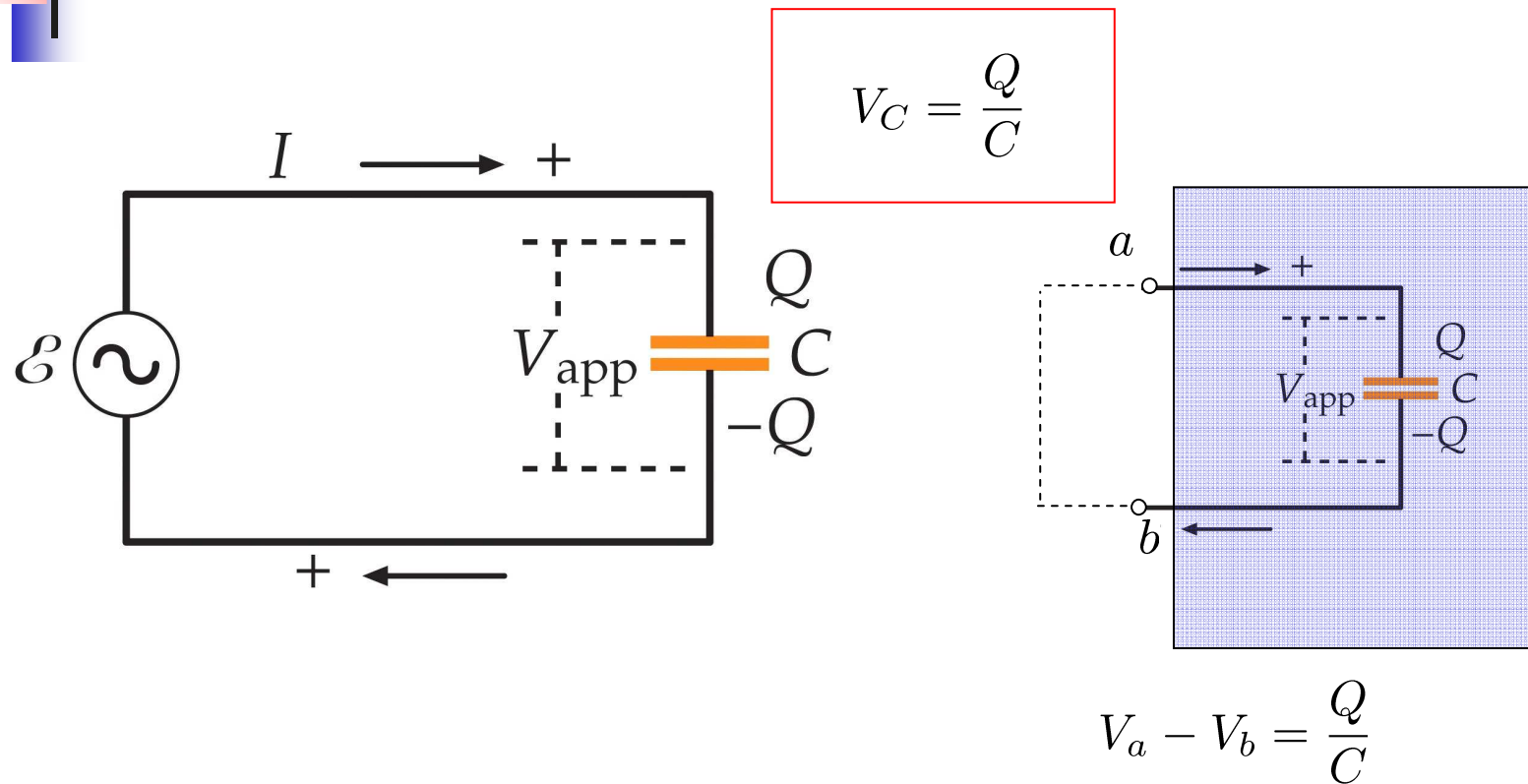

$$V_C = \mathcal{E} = V_{C,\max} \cos \omega t$$

$$Q = V_C C = V_{C,\max} C \cos \omega t$$

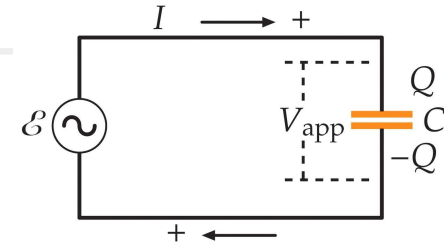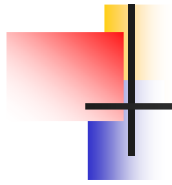
$$I = \frac{dQ}{dt} = -\omega \underbrace{V_{C,\max} C}_{I_{\max}} \sin \omega t = I_{\max} \cos(\omega t + \pi/2)$$



$$V_C = \mathcal{E} = V_{C,\max} \cos \omega t$$

$$I = -\omega V_{C,\max} C \sin \omega t = I_{\max} \cos(\omega t + \pi/2)$$

Desfassament
Potencial retrassat

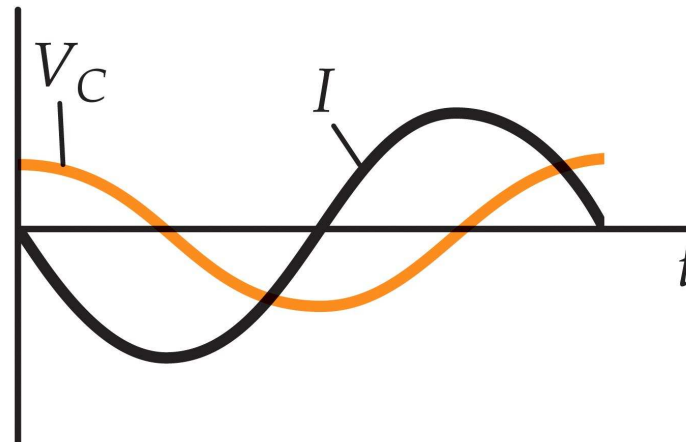



$$I_{\max} = \omega C V_{C,\max} = \frac{V_{C,\max}}{\frac{1}{\omega C}} \equiv \frac{V_{C,\max}}{X_C}$$

Equivalentement

$$I = I_{\max} \cos(\omega t)$$
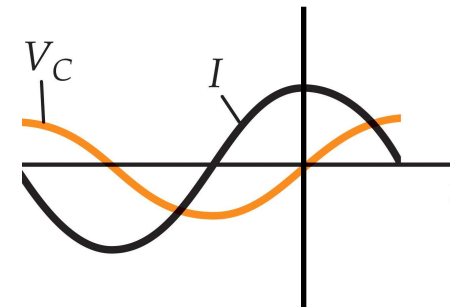
$$V_C = V_{C,\max} \cos(\omega t - \pi/2)$$



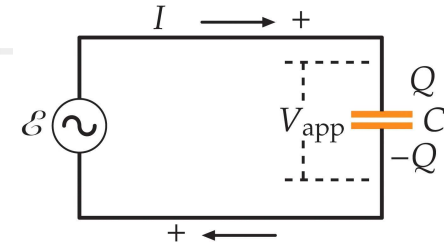

$$X_C = \frac{1}{\omega C}$$

29-30

DEFINITION—CAPACITIVE REACTANCE

$$I_{\max} = \frac{V_{C,\max}}{X_C}$$

$$I_{\text{ef}} = \frac{V_{C,\text{ef}}}{X_C}$$

$$P \equiv V_C I = -V_{C,\max} I_{\max} \cos \omega t \sin \omega t \Rightarrow P_m = 0$$

Representació amb nombres complexos

Fórmula d'Euler

$$e^{i\theta} = \cos \theta + i \sin \theta \quad \left\{ \begin{array}{l} \cos \theta = \operatorname{Re} (e^{i\theta}) \\ \sin \theta = \operatorname{Im} (e^{i\theta}) \end{array} \right.$$

Nombre complexe

$$z = a + ib = r e^{i\theta}$$


mòdul

$$r = \sqrt{a^2 + b^2}$$

fase

$$\tan \theta = \frac{b}{a}$$

Pla complexe

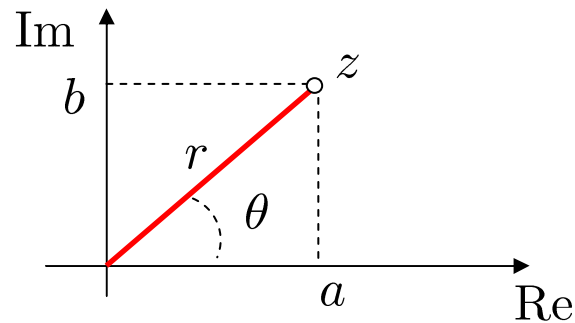



$$V = V_{\max} \cos(\omega t + \varphi_0) = \operatorname{Re} (V_{\max} e^{i\varphi_0} e^{i\omega t})$$

$$\curvearrowright \hat{V} = V_{\max} e^{i\varphi_0} \quad \text{amplada complexa (o fasor)}$$

$$\left. \begin{array}{l} V = \operatorname{Re} (\hat{V} e^{i\omega t}) \\ I = \operatorname{Re} (\hat{I} e^{i\omega t}) \\ \dots \end{array} \right\} \text{fase temporal comuna } e^{i\omega t}$$

A vegades, abús de notació

$$V = \hat{V} e^{i\omega t}$$

$$I = \hat{I} e^{i\omega t}$$

Impedàncies complexes


$$Z = \frac{\hat{V}e^{i\omega t}}{\hat{I}e^{i\omega t}} = \frac{\hat{V}}{\hat{I}}$$

la fase de Z és el desfassament entre potencial i intensitat

$\varphi > 0 \Rightarrow V$ adelantat

$\varphi < 0 \Rightarrow V$ retrassat

bobina

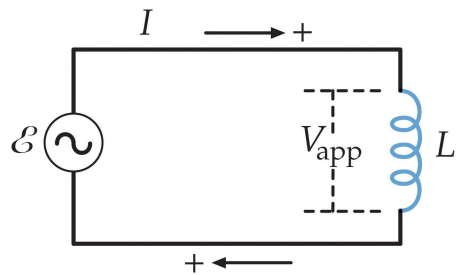


$$V = V_{\max} \cos \omega t = \text{Re} (V_{\max} e^{i\omega t})$$


$$I = \frac{V_{\max}}{\omega L} \cos(\omega t - \pi/2) = \text{Re} \left(\frac{V_{\max}}{\omega L} e^{-i\pi/2} e^{i\omega t} \right)$$

$$e^{-i\pi/2} = -i = \frac{1}{i}$$

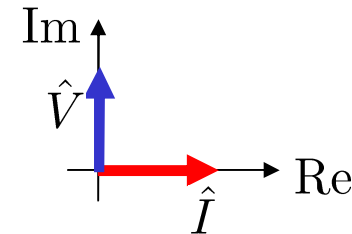
$$Z = \frac{\hat{V}}{\hat{I}} = i\omega L$$




condensador

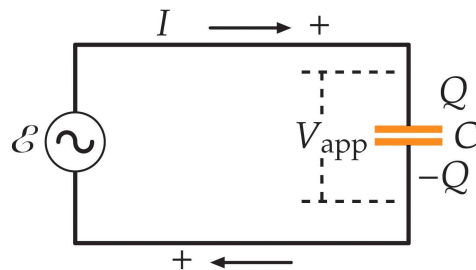
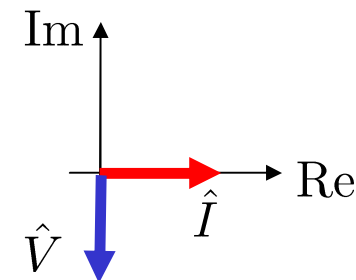
$$Z = \frac{\hat{V}}{\hat{I}} = \frac{1}{i\omega C} = -i \frac{1}{\omega C}$$



Resistència

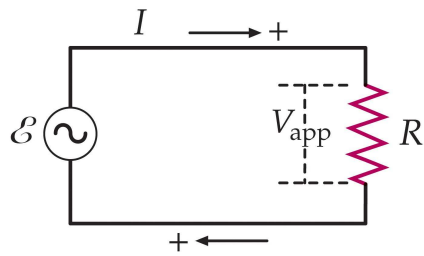

$$Z = \frac{\hat{V}}{\hat{I}} = R$$

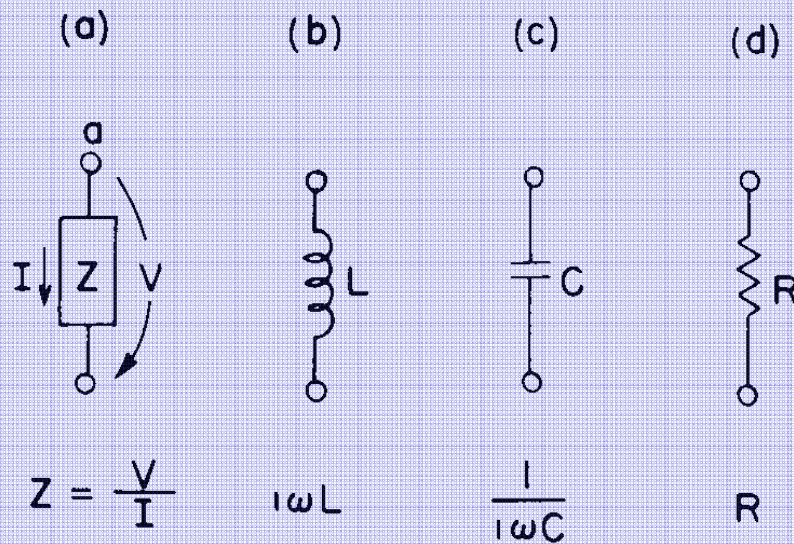
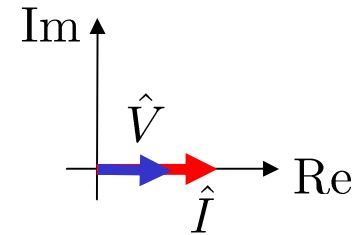


Fig. 22-4. The ideal lumped circuit elements (passive).

Impedància general

$$Z = R + iX$$


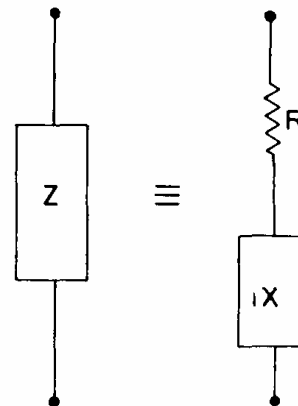
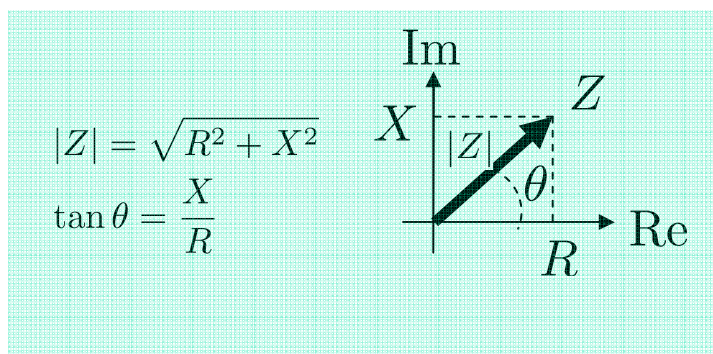



Fig. 22-17. Any impedance is equivalent to a series combination of a pure resistance and a pure reactance.

Associació d'impedàncies

Sèrie

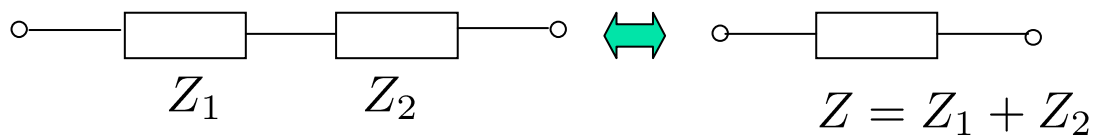

Paral.lel

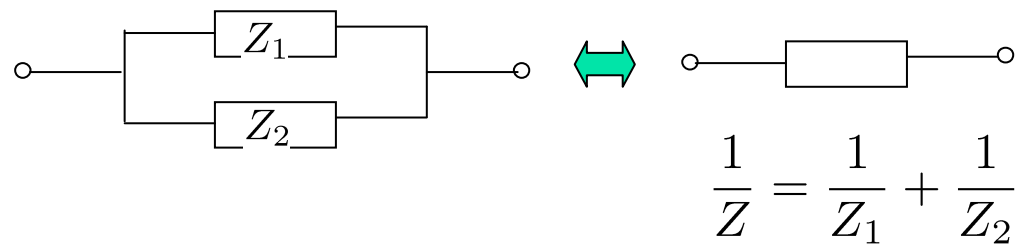

Lleis de Kirchhoff

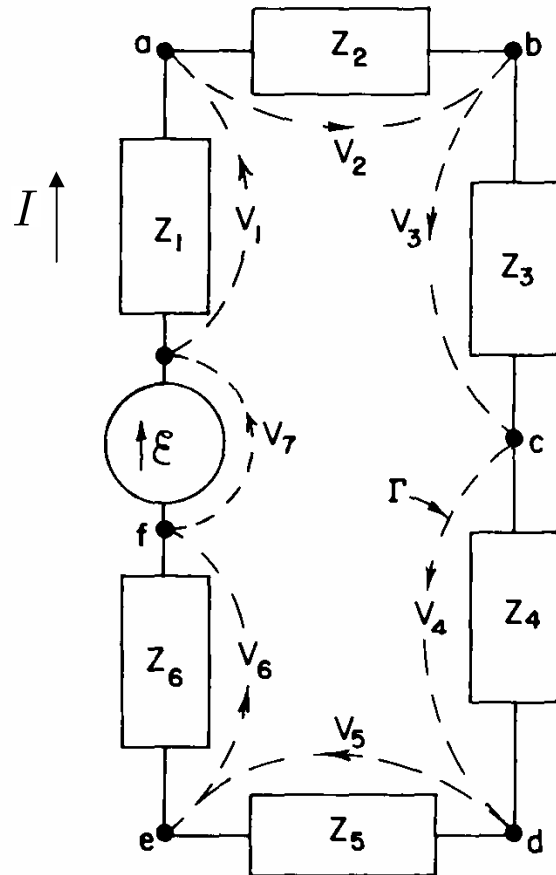


Fig. 22-9. The sum of the voltage drops around any closed path is zero.

$$-Z_1 \hat{I} - Z_2 \hat{I} - Z_3 \hat{I} - Z_4 \hat{I} - Z_5 \hat{I} + Z_6 \hat{I} + \hat{\mathcal{E}} = 0$$

$$\hat{I} = \frac{\hat{\mathcal{E}}}{\sum_i Z_i} \quad I = \text{Re} \left(\hat{I} e^{i\omega t} \right)$$

$$\frac{\hat{\mathcal{E}}}{\hat{I}} = \sum_i Z_i$$

Potència a partir de la impedancia

$$P = VI$$


$$\hat{V} = Z\hat{I} = (R + iX)\hat{I} \quad \rightarrow \quad V = \operatorname{Re}((R + iX)I_0 e^{i\omega t})$$

$$= RI_0 \cos \omega t - XI_0 \sin \omega t$$

$$P = VI = RI_0^2 \cos^2 \omega t - XI_0^2 \sin \omega t \cos \omega t \quad \rightarrow \quad P_m = R \frac{I_0^2}{2}$$

$$P_m = RI_e^2$$

però $R = |Z| \cos \theta$

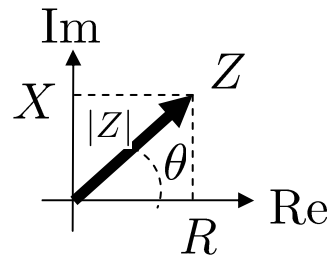

també $\hat{V} = Z\hat{I} \quad \rightarrow \quad |\hat{V}| = |Z||\hat{I}|$

$$V_0 = |Z|I_0$$


$$P_m = \frac{V_0 I_0}{2} \cos \theta$$

$$P_m = V_e I_e \cos \theta$$

Factor de potència 21

Circuits simples


RC

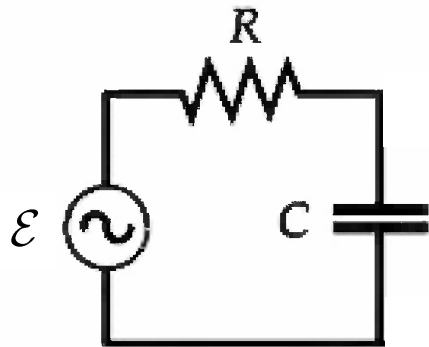

$$Z = R + \frac{1}{iC\omega} = R - i\frac{1}{C\omega}$$

$$|Z| = \sqrt{R^2 + \frac{1}{C^2\omega^2}}$$
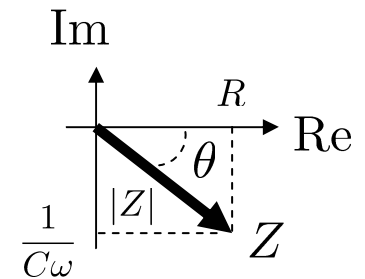
$$\theta = -\text{atan}\left(\frac{\frac{1}{C\omega}}{R}\right)$$





$$\hat{I} = \frac{\hat{\mathcal{E}}}{Z}$$



$$I = \text{Re}\left(\hat{I} e^{i\omega t}\right)$$

$$\hat{V}_R = R\hat{I}$$

$$\hat{V}_C = \frac{1}{iC\omega}\hat{I}$$
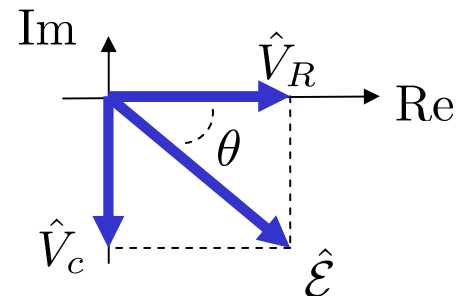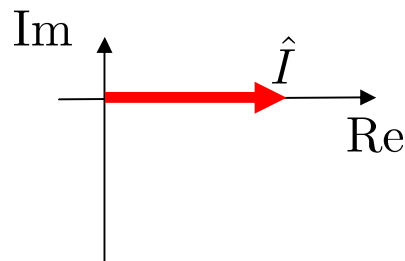
$$\hat{\mathcal{E}} = \hat{V}_R + \hat{V}_C$$



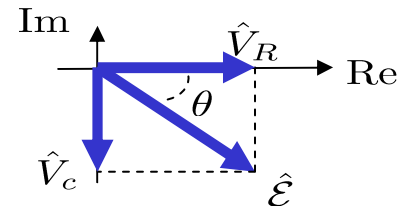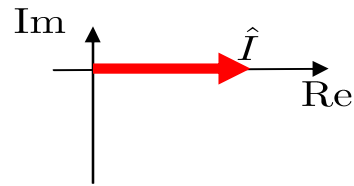

$$I = I_{\max} \cos \omega t$$

$$I_{\max} = \frac{\mathcal{E}_{\max}}{|Z|} = \frac{\mathcal{E}_{\max}}{\sqrt{R^2 + \frac{1}{C^2 \omega^2}}}$$

$$\mathcal{E} = \mathcal{E}_{\max} \cos(\omega t - \theta)$$

$$\mathcal{E}_{\max}$$


$$V_R = V_{R,\max} \cos(\omega t)$$

$$V_{R,\max} = RI_{\max} = \frac{R\mathcal{E}_{\max}}{\sqrt{R^2 + \frac{1}{C^2 \omega^2}}}$$

$$V_C = V_{C,\max} \cos(\omega t - \pi/2)$$

$$V_{C,\max} = \frac{1}{C\omega} I_{\max} = \frac{\frac{1}{C\omega} \mathcal{E}_{\max}}{\sqrt{R^2 + \frac{1}{C^2 \omega^2}}}$$

Filtres

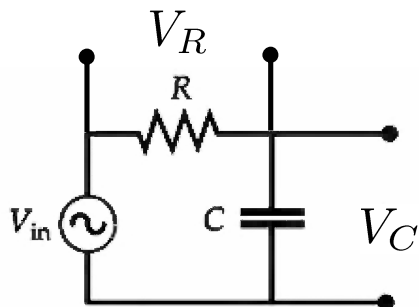

$$\omega \rightarrow 0 \quad \begin{cases} V_{R,\max} \rightarrow 0 \\ V_{C,\max} \rightarrow \mathcal{E}_{\max} \end{cases} \quad \text{Passa baixa}$$


$$\omega \rightarrow \infty \quad \begin{cases} V_{R,\max} \rightarrow \mathcal{E}_{\max} \\ V_{C,\max} \rightarrow 0 \end{cases} \quad \text{Passa alta}$$



RL

Exercici


RCL

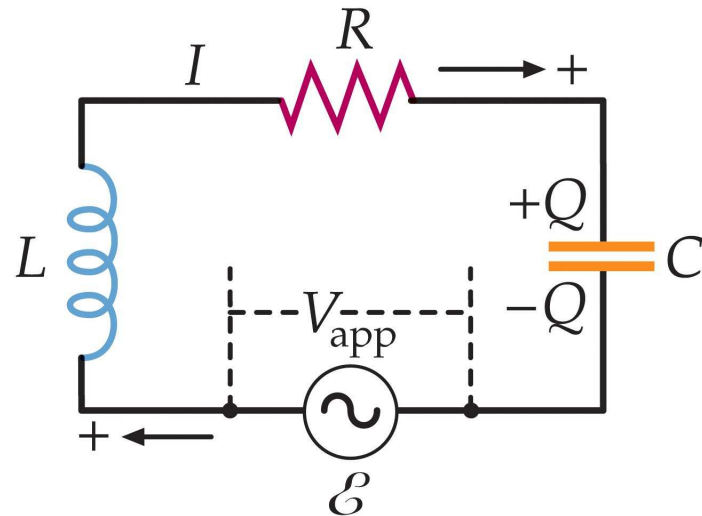

$$Z = R + i \left(L\omega - \frac{1}{C\omega} \right)$$

$$|Z| = \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2}$$
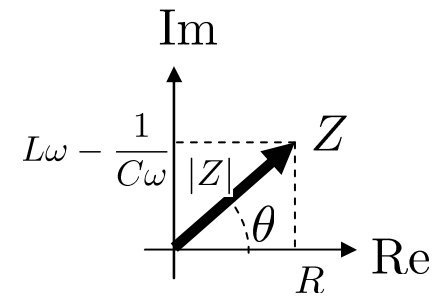
$$\theta = \text{atan} \left(\frac{L\omega - \frac{1}{C\omega}}{R} \right)$$





$$\hat{I} = \frac{\hat{\mathcal{E}}}{Z}$$




$$\hat{V}_R = R\hat{I}$$

$$\hat{V}_C = \frac{1}{iC\omega}\hat{I}$$

$$\hat{V}_L = iL\omega\hat{I}$$
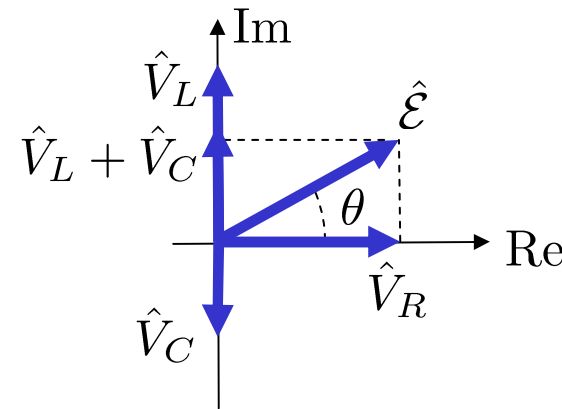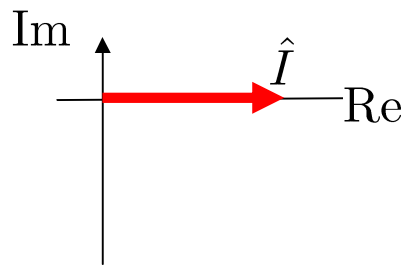
$$\hat{\mathcal{E}} = \hat{V}_R + \hat{V}_C + \hat{V}_L$$



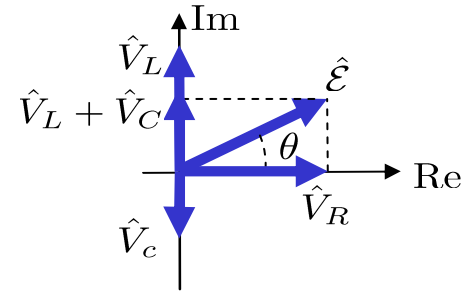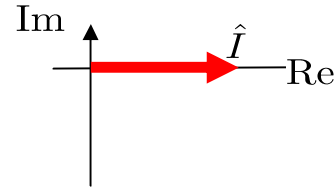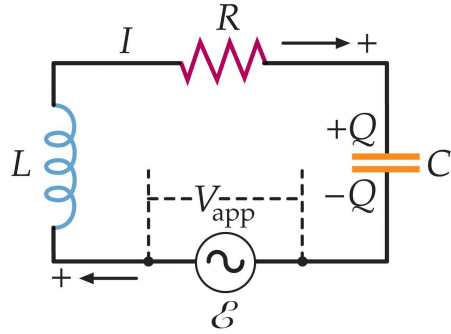

$$I = I_{\max} \cos \omega t$$

$$I_{\max} = \frac{\mathcal{E}_{\max}}{|Z|} = \frac{\mathcal{E}_{\max}}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$\mathcal{E} = \mathcal{E}_{\max} \cos(\omega t + \theta)$$

$$\mathcal{E}_{\max}$$

$$V_R = V_{R,\max} \cos(\omega t)$$

$$V_{R,\max} = RI_{\max} = \frac{R\mathcal{E}_{\max}}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$V_C = V_{C,\max} \cos(\omega t - \pi/2)$$

$$V_{C,\max} = \frac{1}{C\omega} I_{\max} = \frac{\frac{1}{C\omega} \mathcal{E}_{\max}}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$V_L = V_{L,\max} \cos(\omega t + \pi/2)$$

$$V_{L,\max} = iL\omega I_{\max} = \frac{L\omega \mathcal{E}_{\max}}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$



$$V_{R,\max} = RI_{\max} = \frac{R\mathcal{E}_{\max}}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$\begin{cases} \omega \rightarrow 0 & V_{R,\max} \rightarrow 0 \\ \omega = \sqrt{\frac{1}{LC}} & V_{R,\max} = \mathcal{E}_{\max} \\ \omega \rightarrow \infty & V_{R,\max} \rightarrow 0 \end{cases}$$

Filtre
"passa banda"

Potència


$$\begin{aligned} P_m &= R \frac{I_{\max}^2}{2} = \frac{R}{2} \frac{\mathcal{E}_{\max}^2}{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} \\ &= \frac{R\mathcal{E}_{\max}^2}{2} \frac{\omega^2}{L^2(\omega^2 - \omega_0^2)^2 + \omega^2 R^2} \end{aligned}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

Ressonància a $\omega = \omega_0$



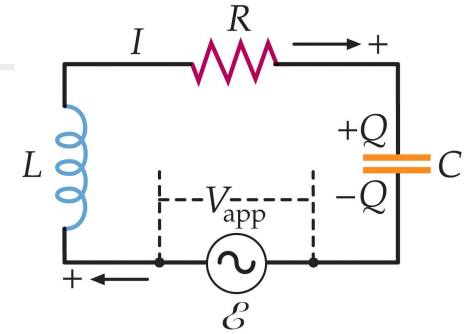
$$P_m = \frac{R\mathcal{E}_{\max}^2}{2} \frac{\omega^2}{L^2(\omega^2 - \omega_0^2) + \omega^2 R^2}$$




$$\omega_0 = \sqrt{\frac{1}{LC}}$$


$$Q = \frac{\omega_0 L}{R}$$
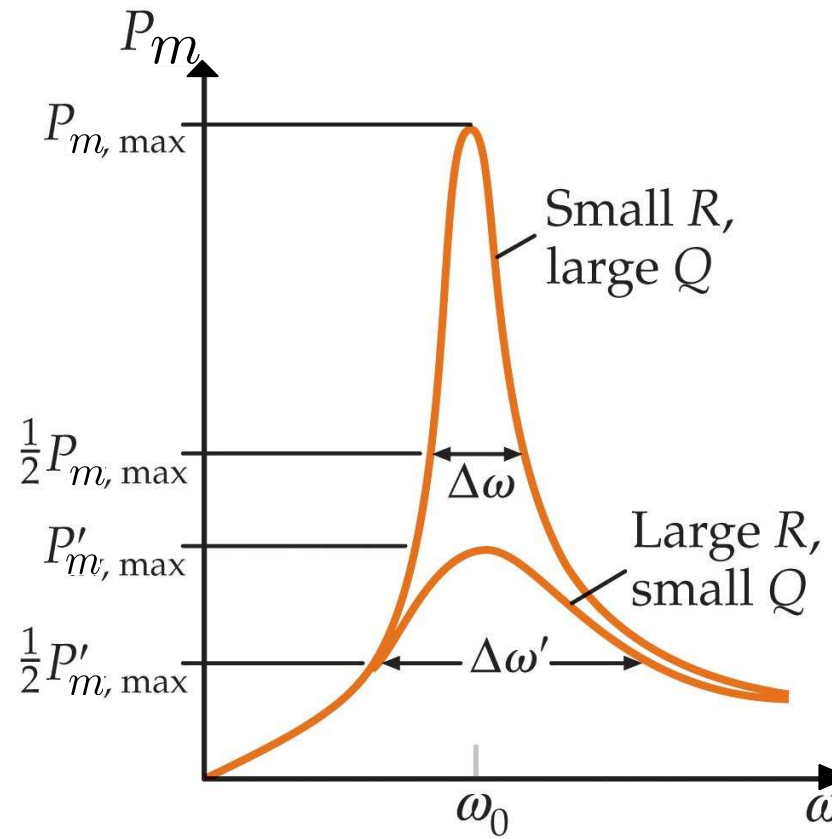
$$\Delta\omega \approx \frac{\omega_0}{Q}$$



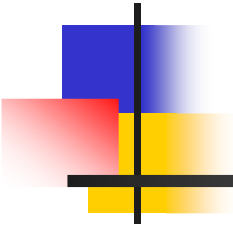

Problems

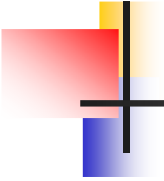


29.1



29.3


29.4



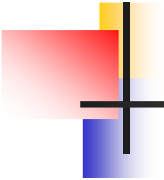


29.5




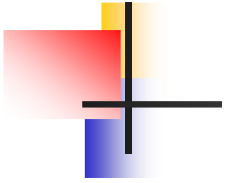


29.37

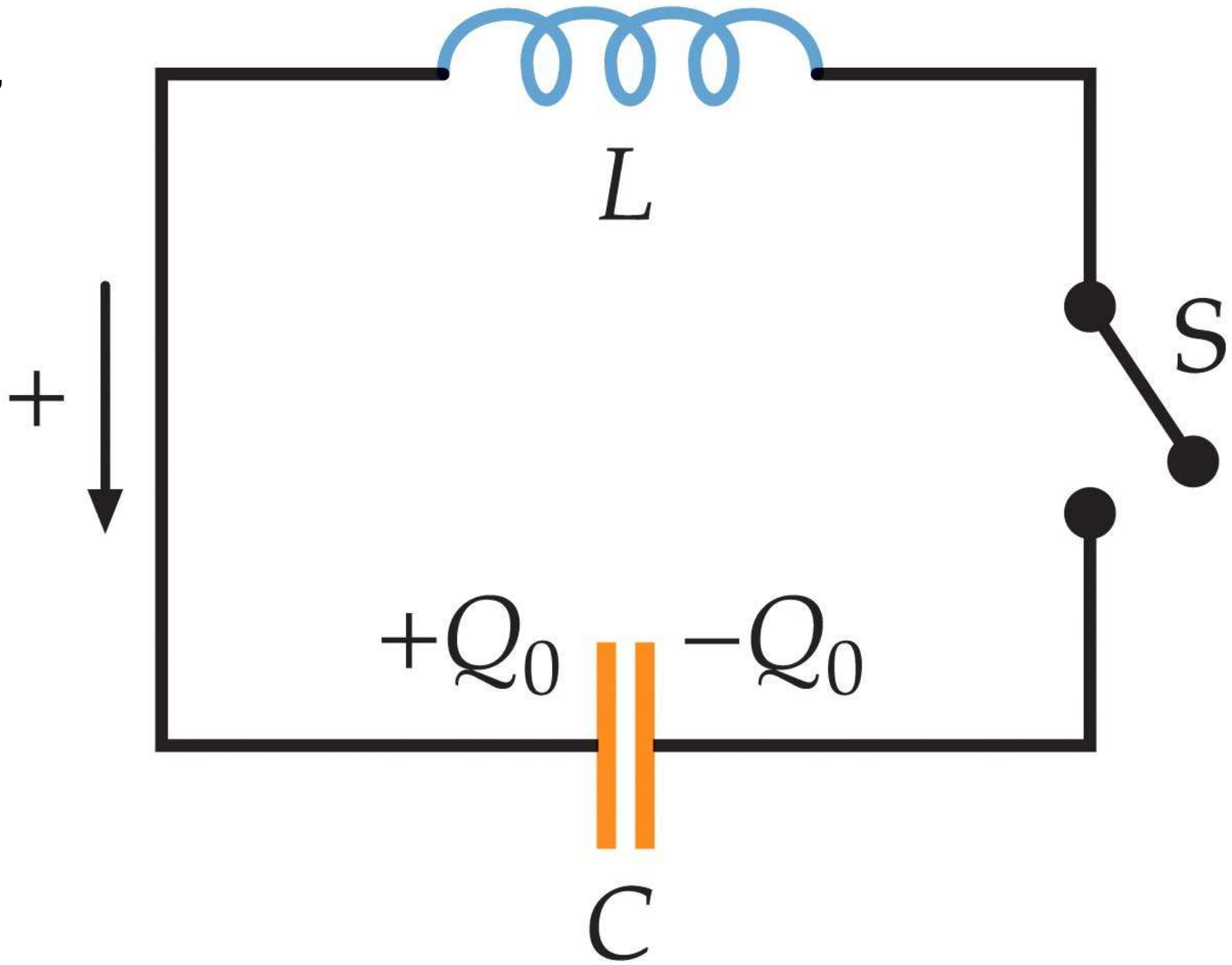


29.40

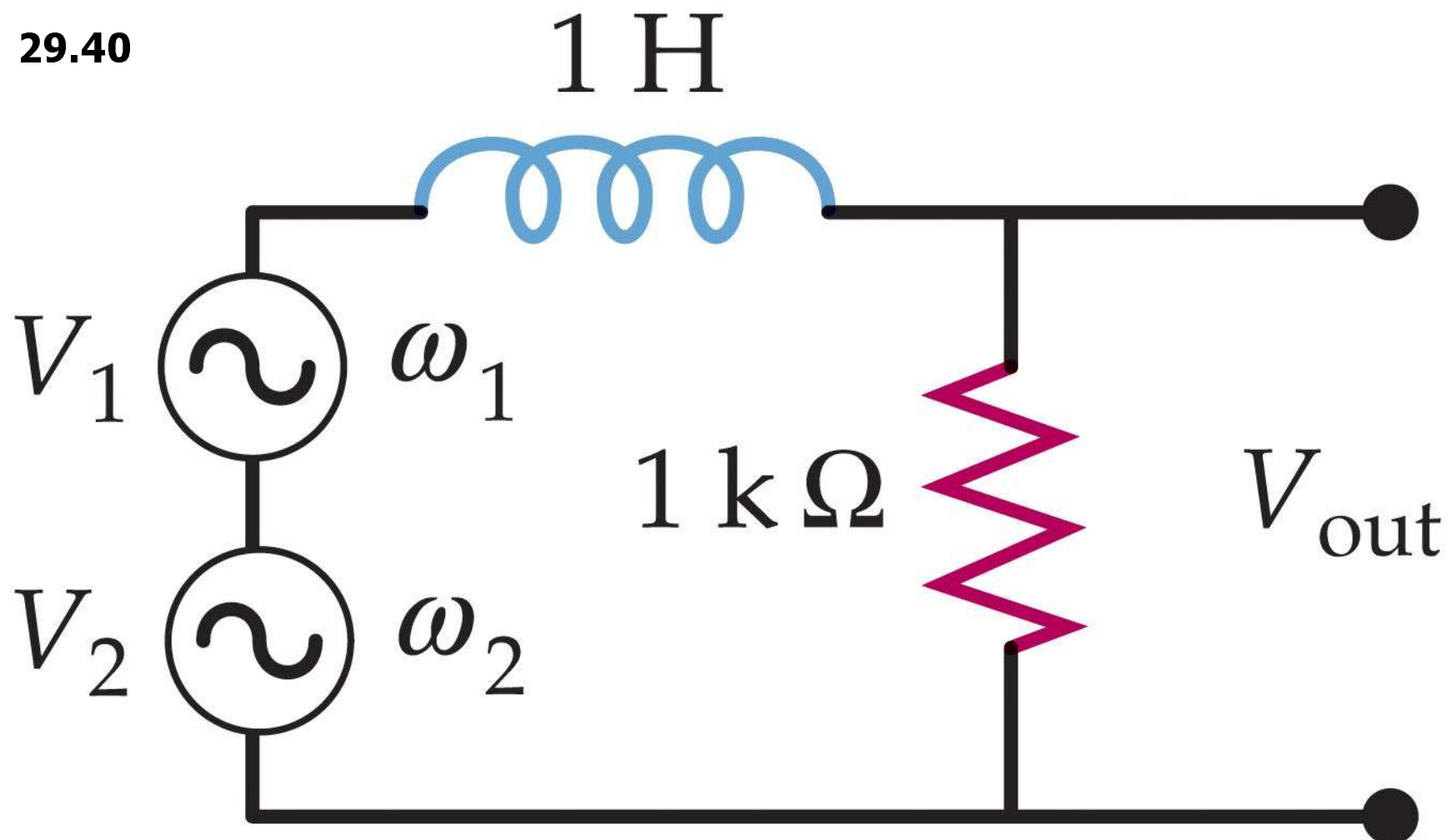


29.44

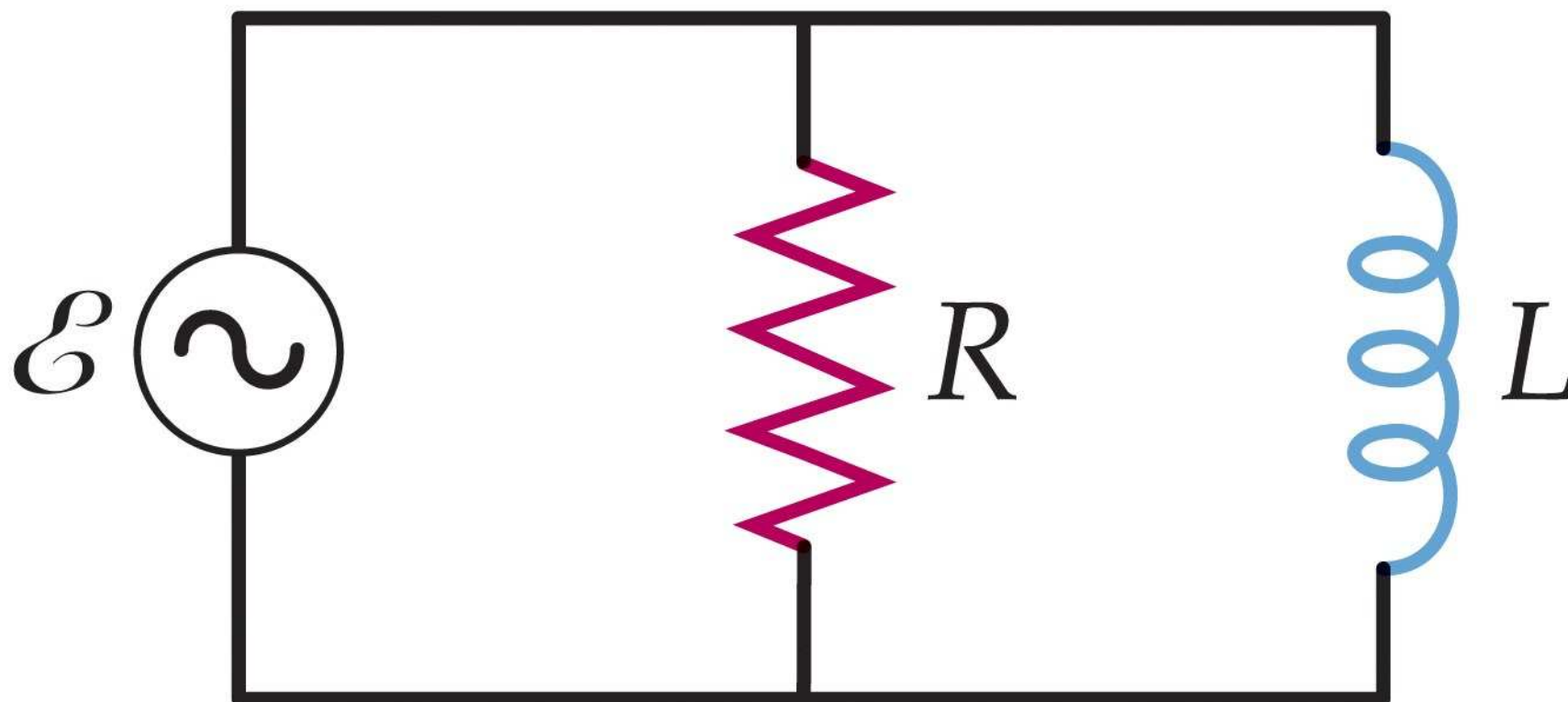


29.45

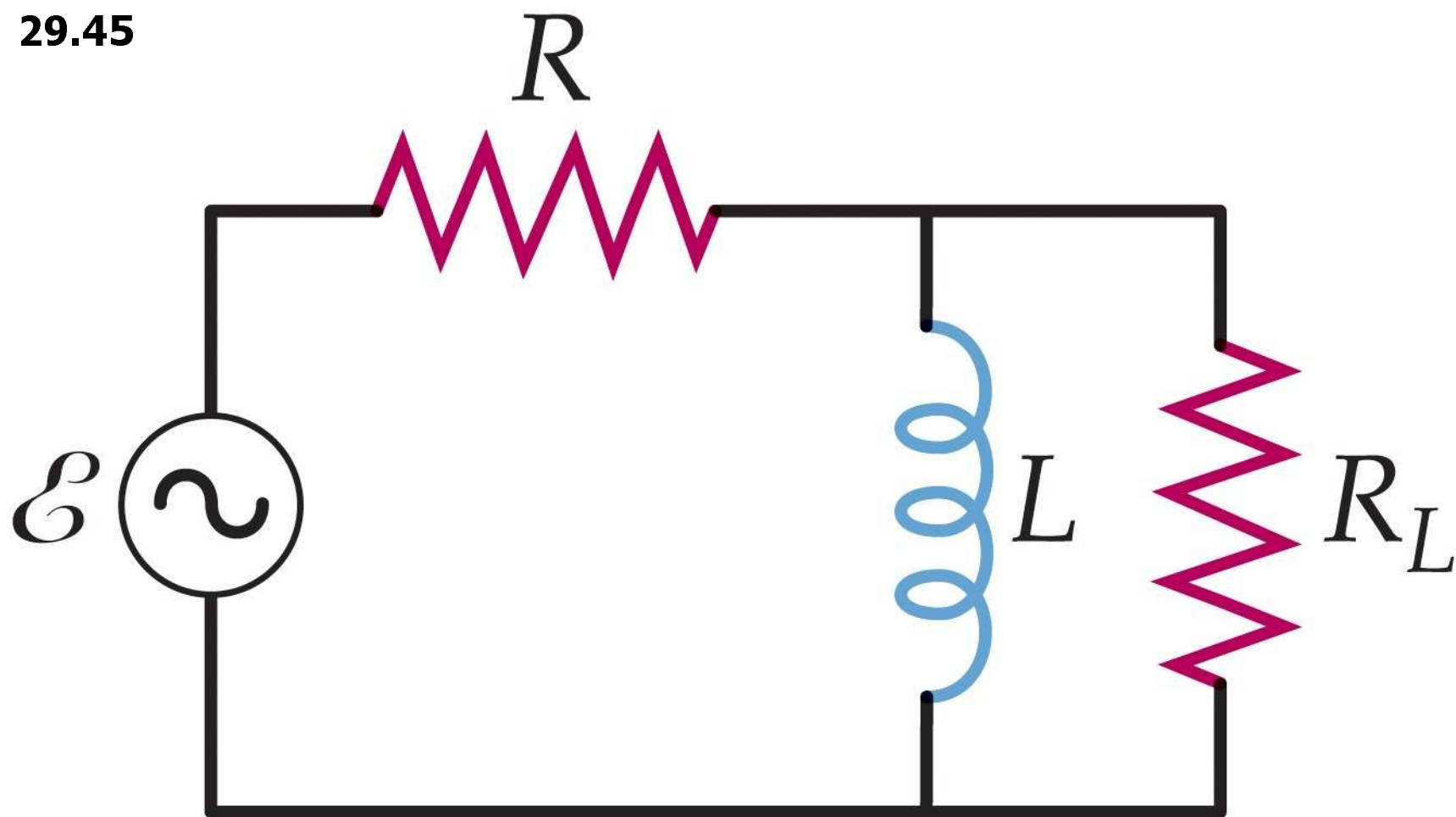

29.46

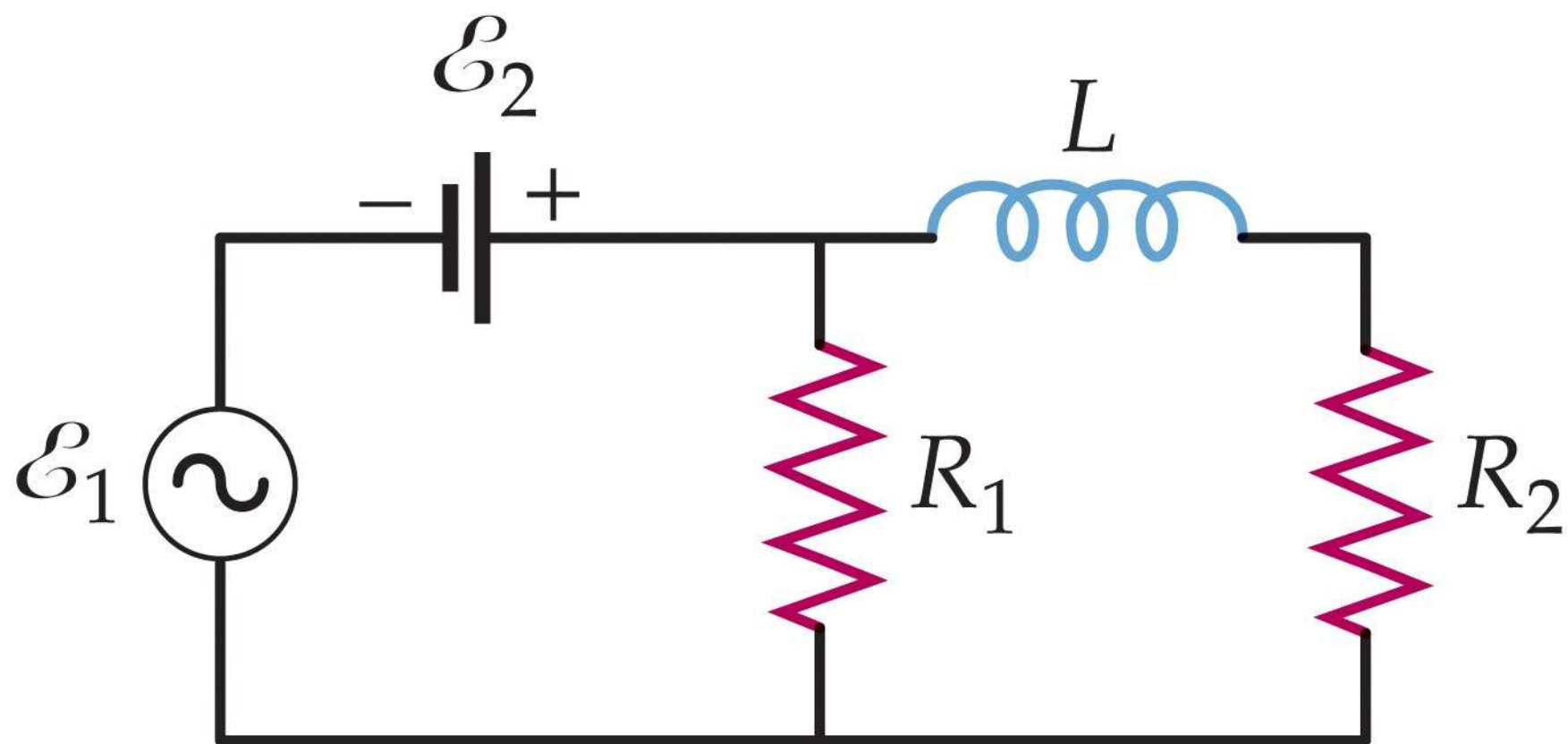

29.48

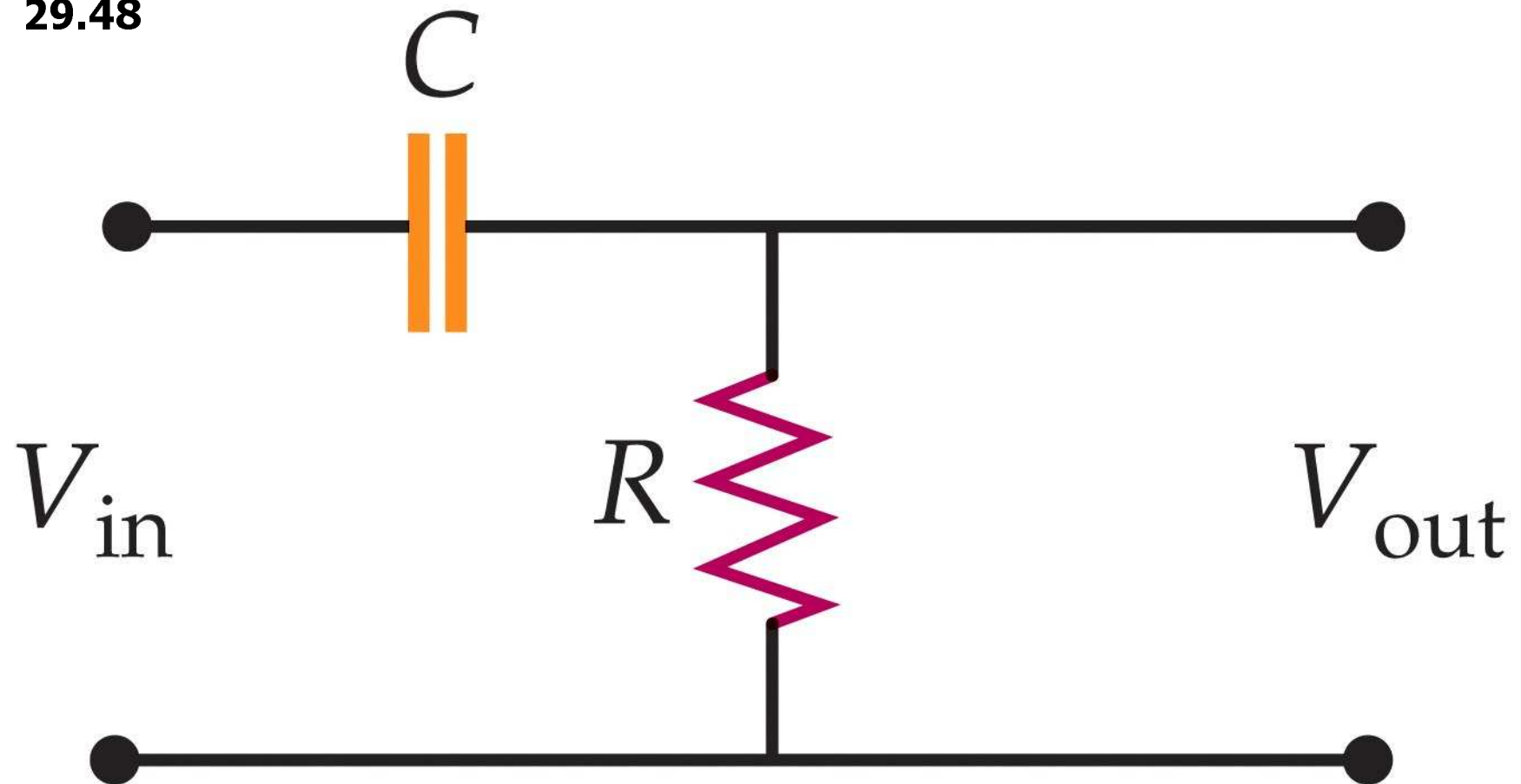

29.55


R

V_{in}


C


V_{out}

29.59

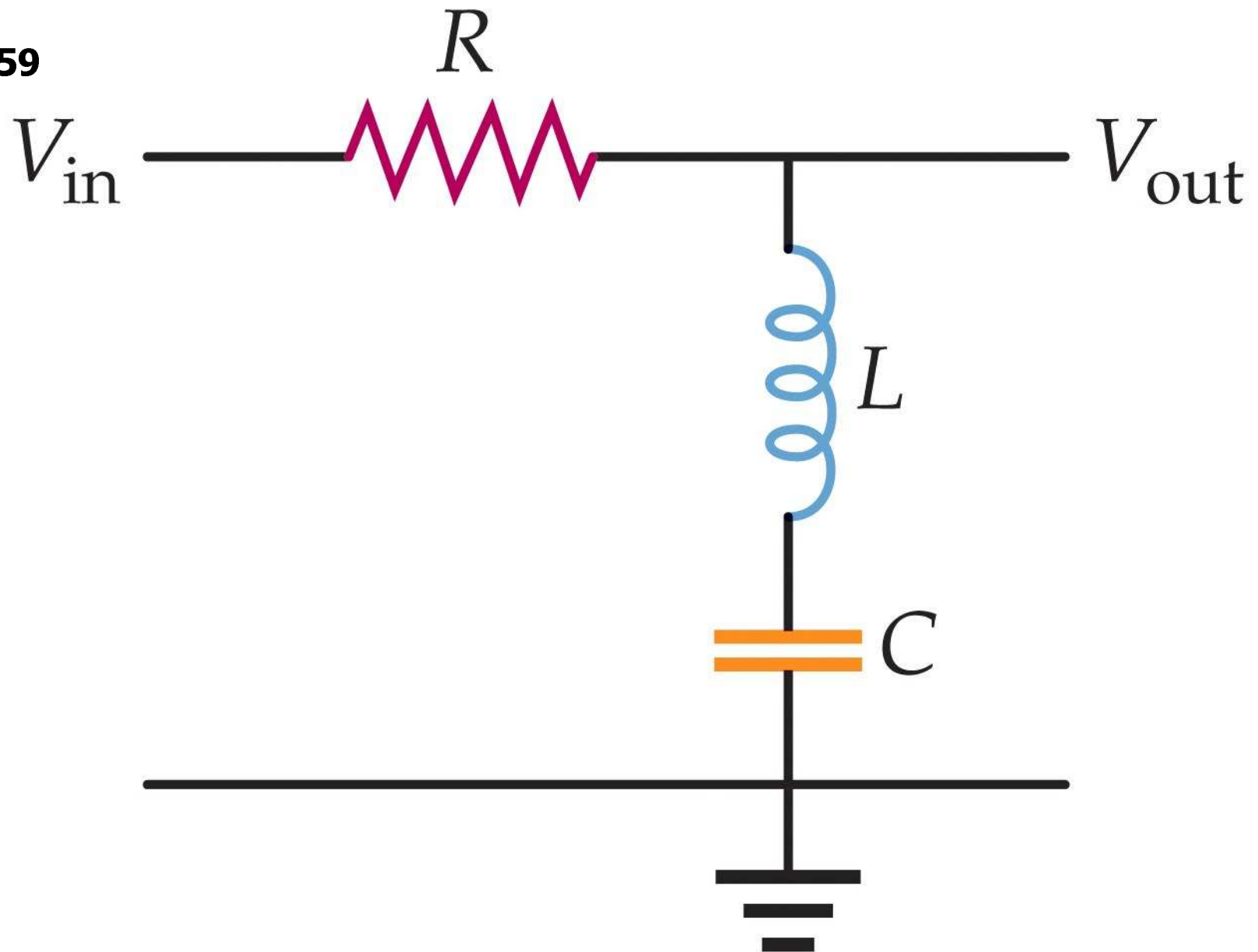


29.62

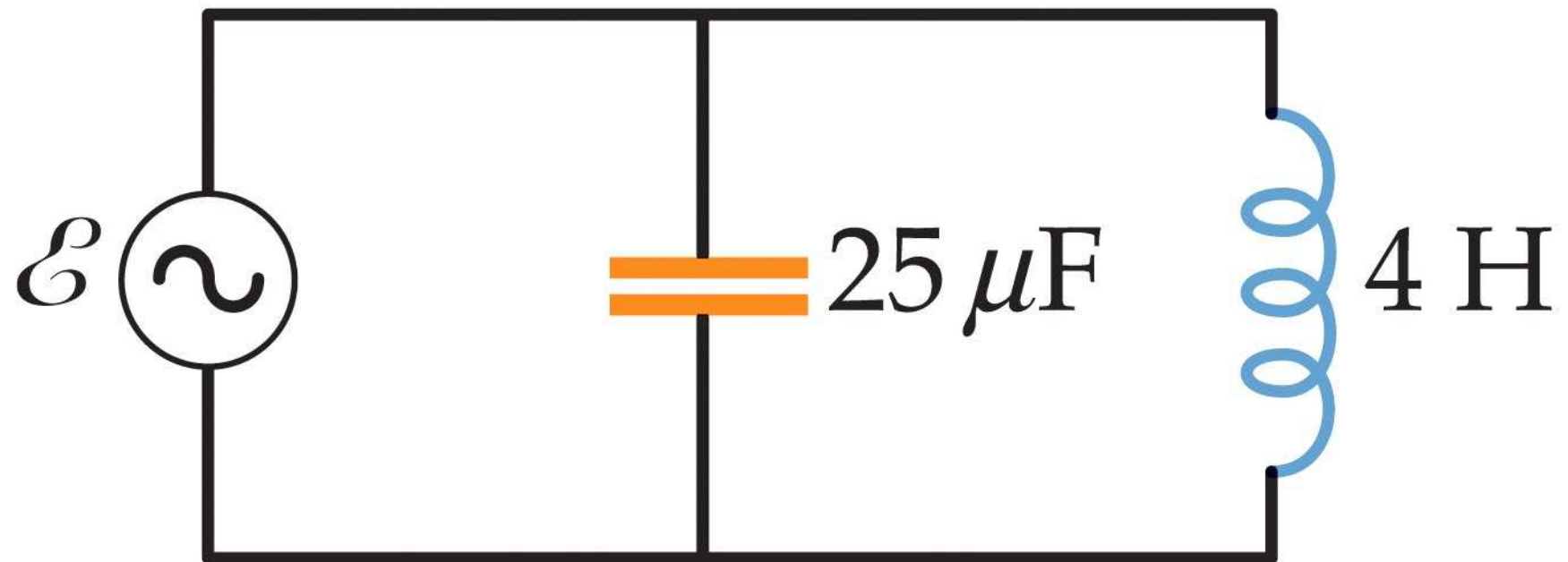


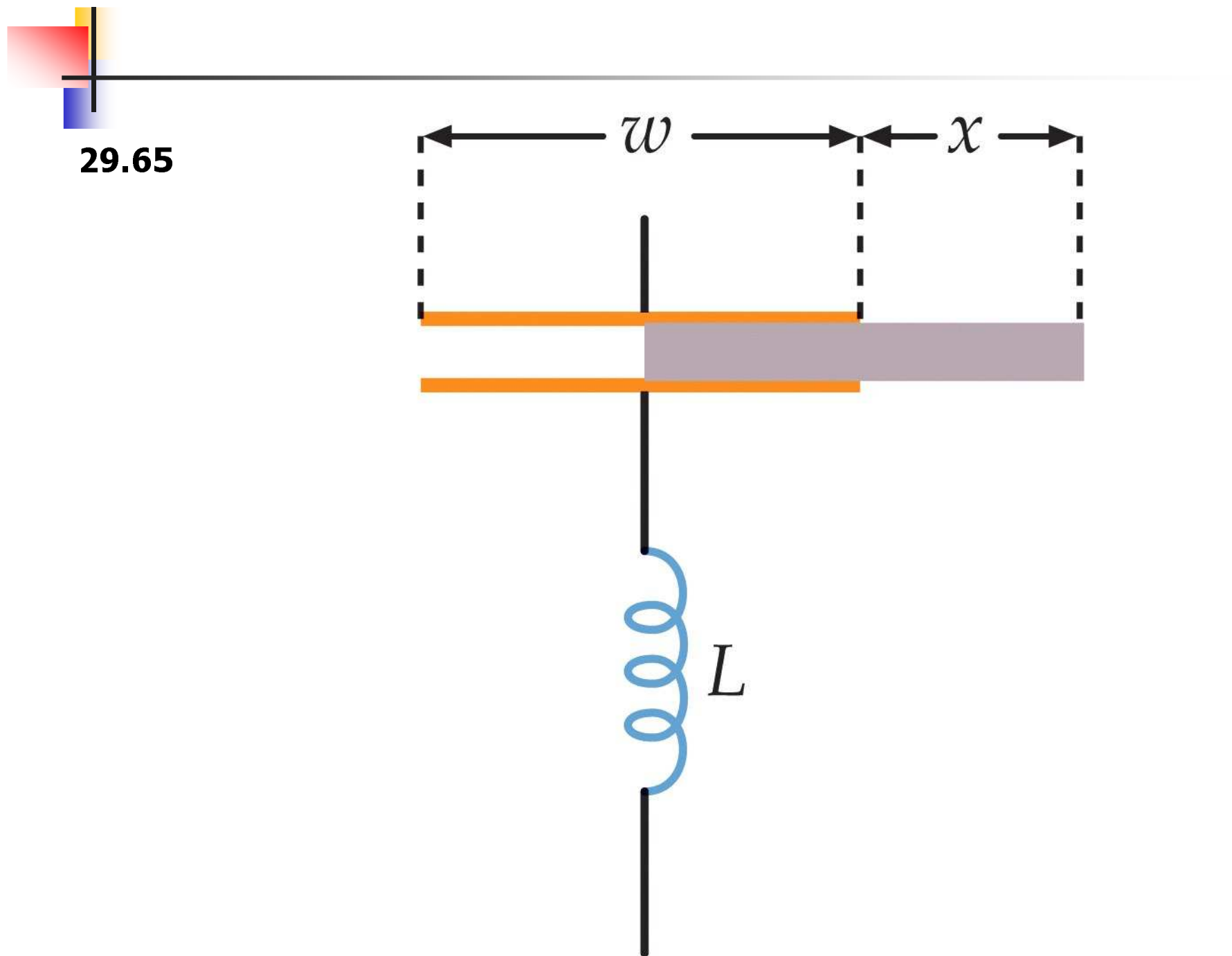


29.79

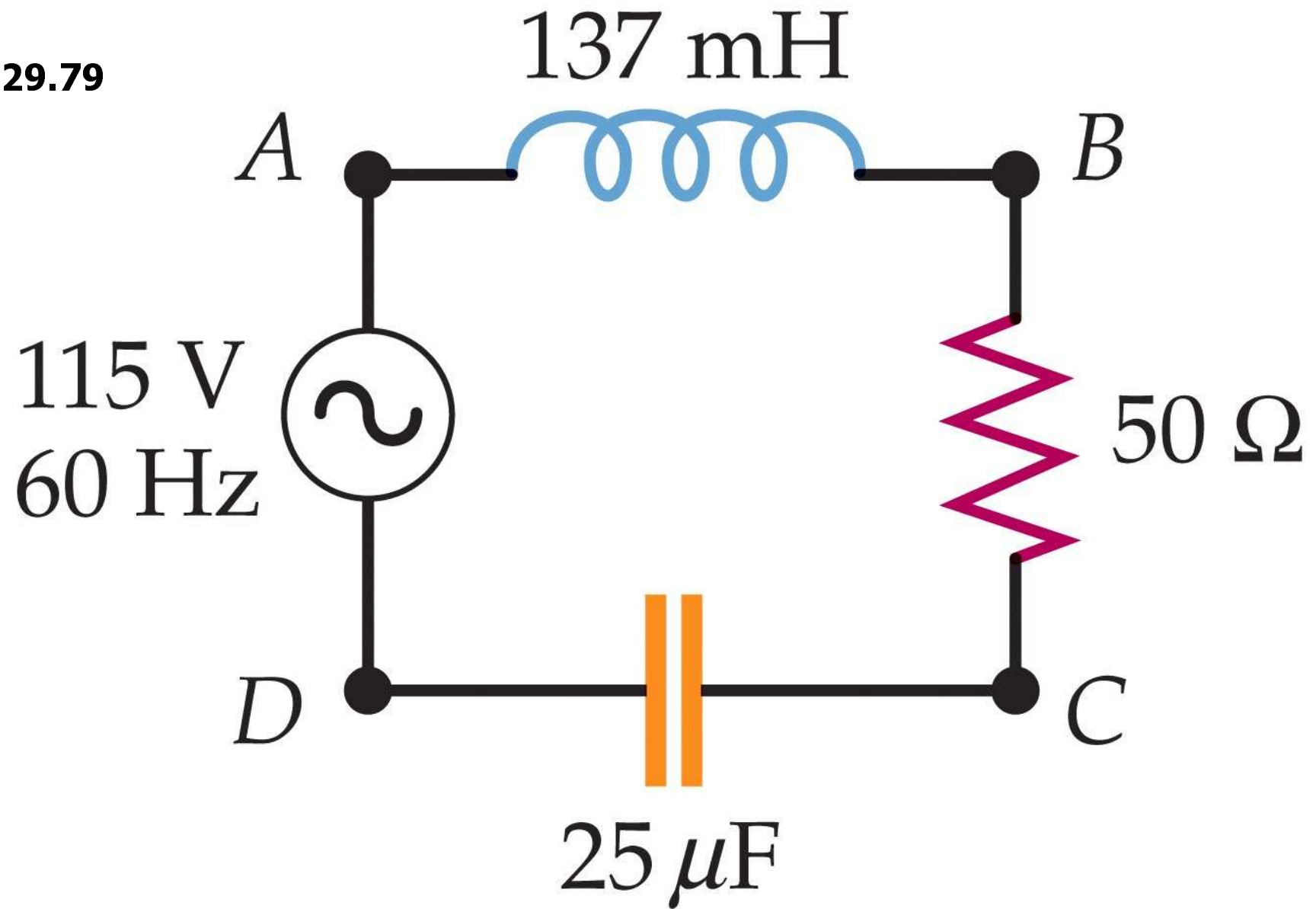


29.89

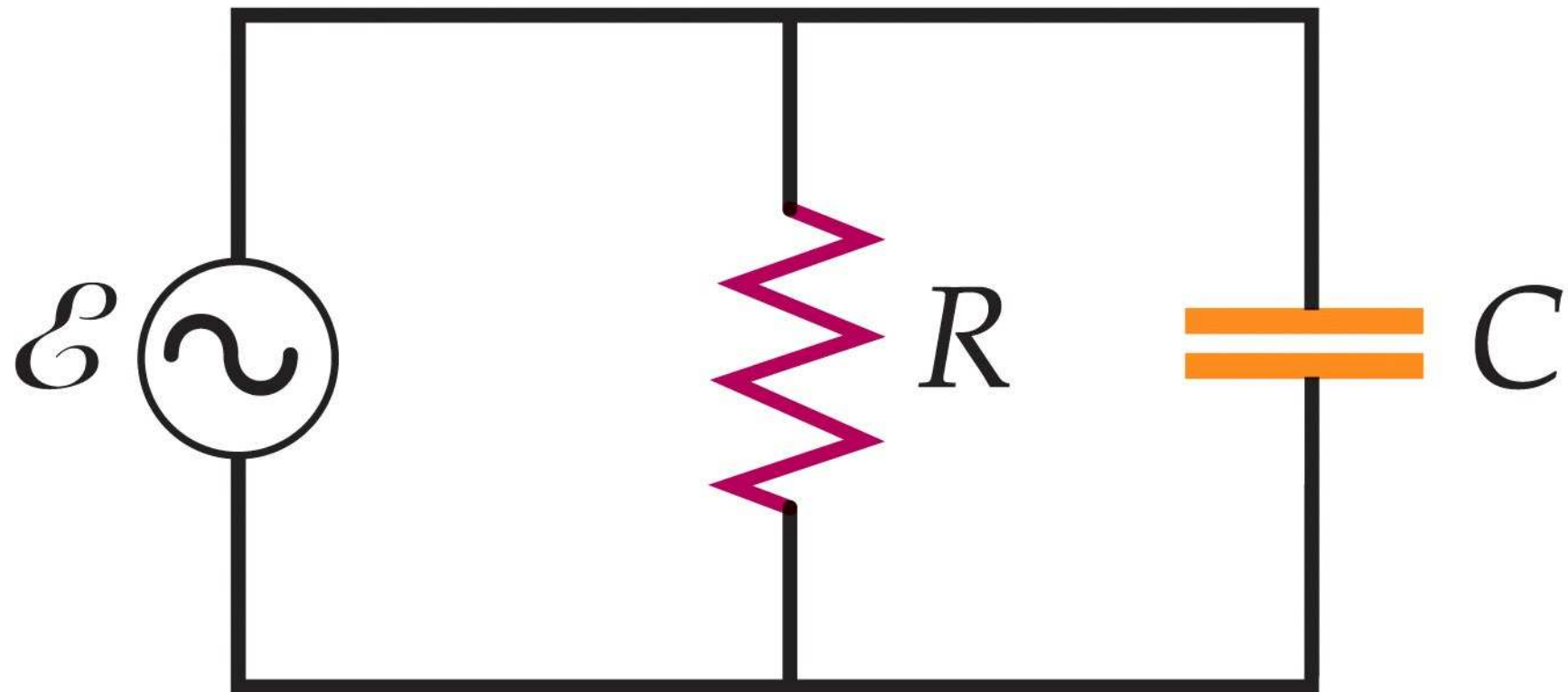


29.90

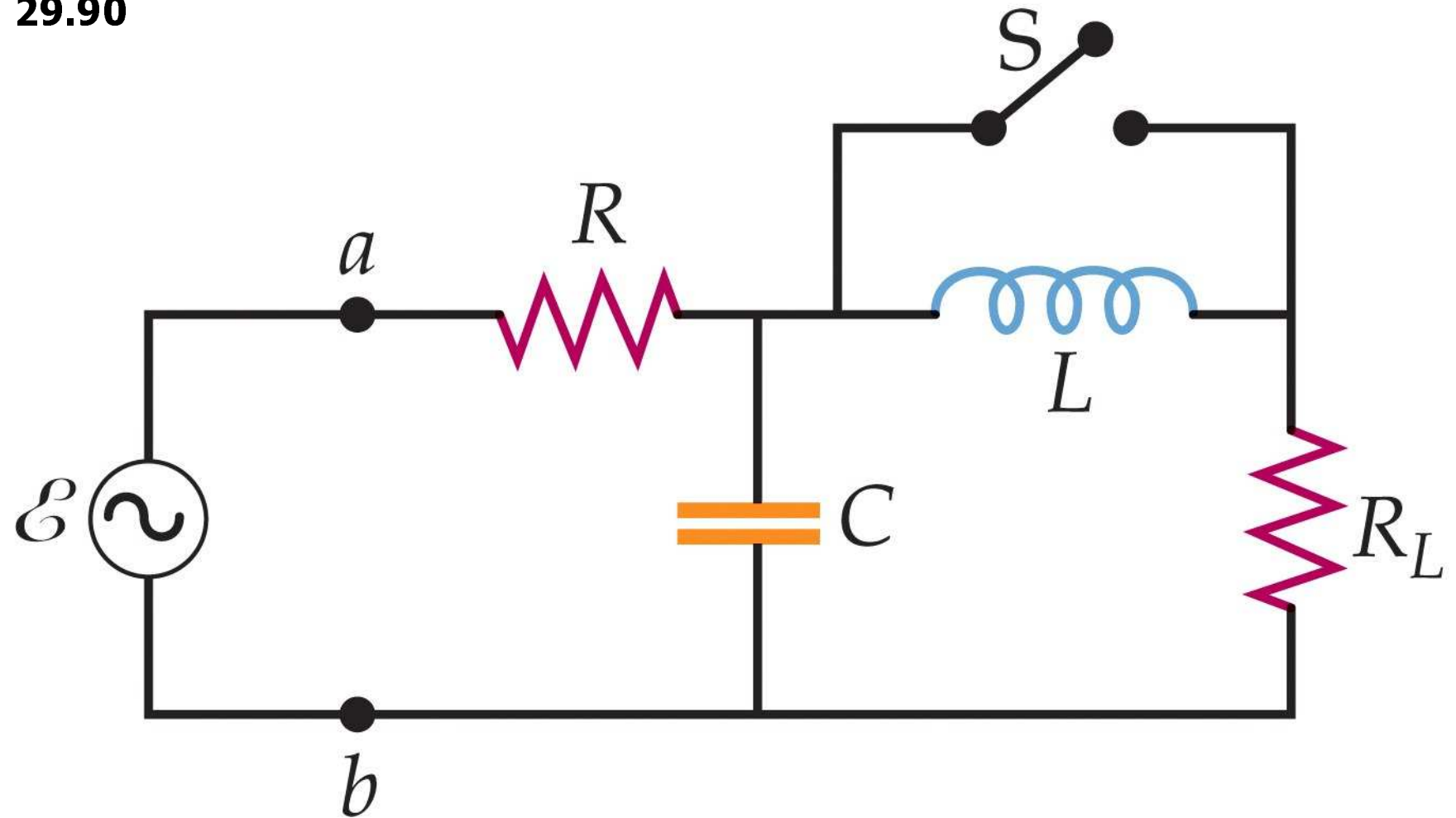


29.91

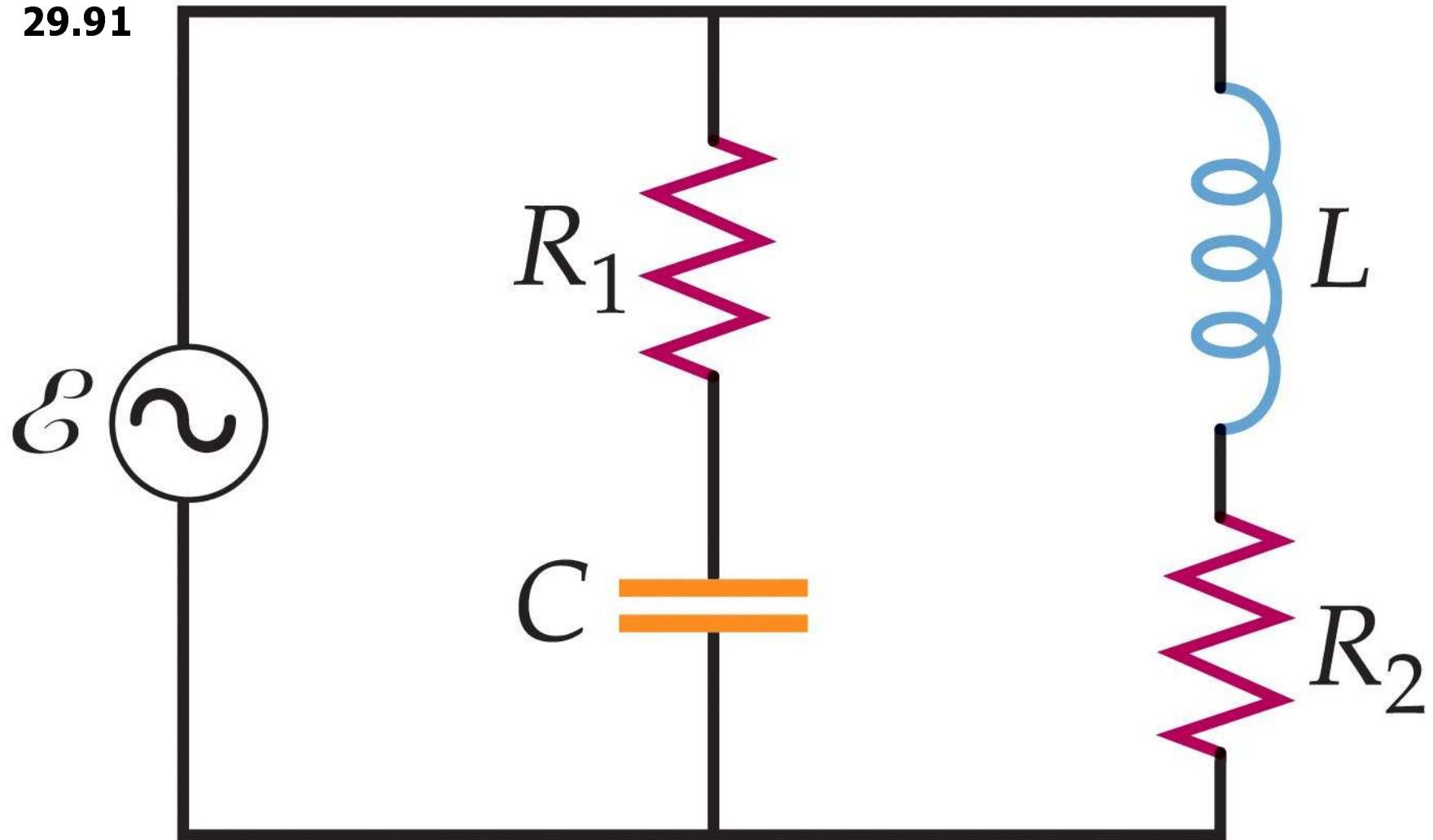



29.96

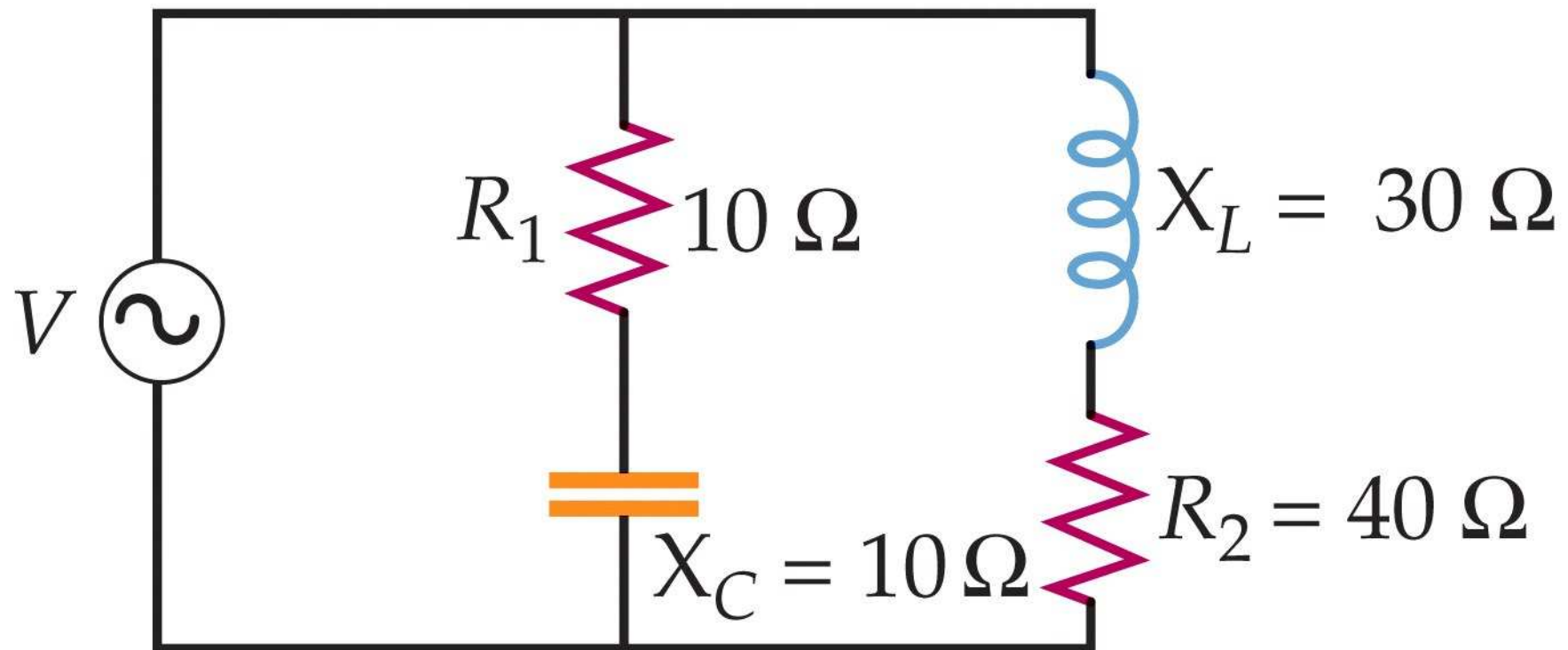

29.117

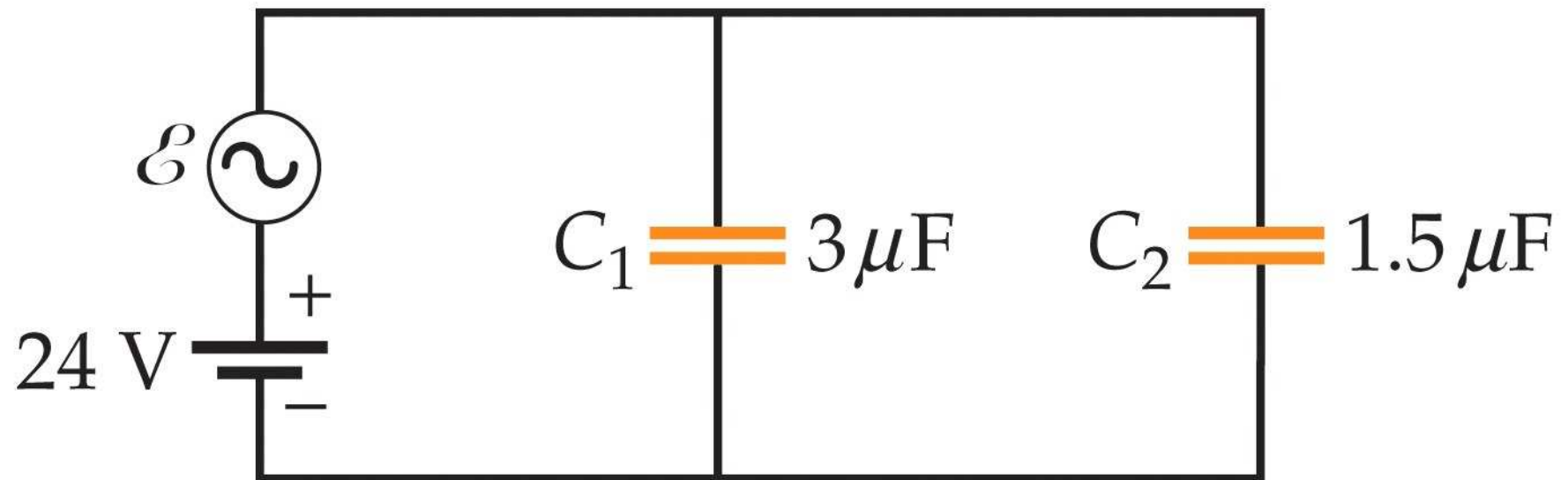

29.118

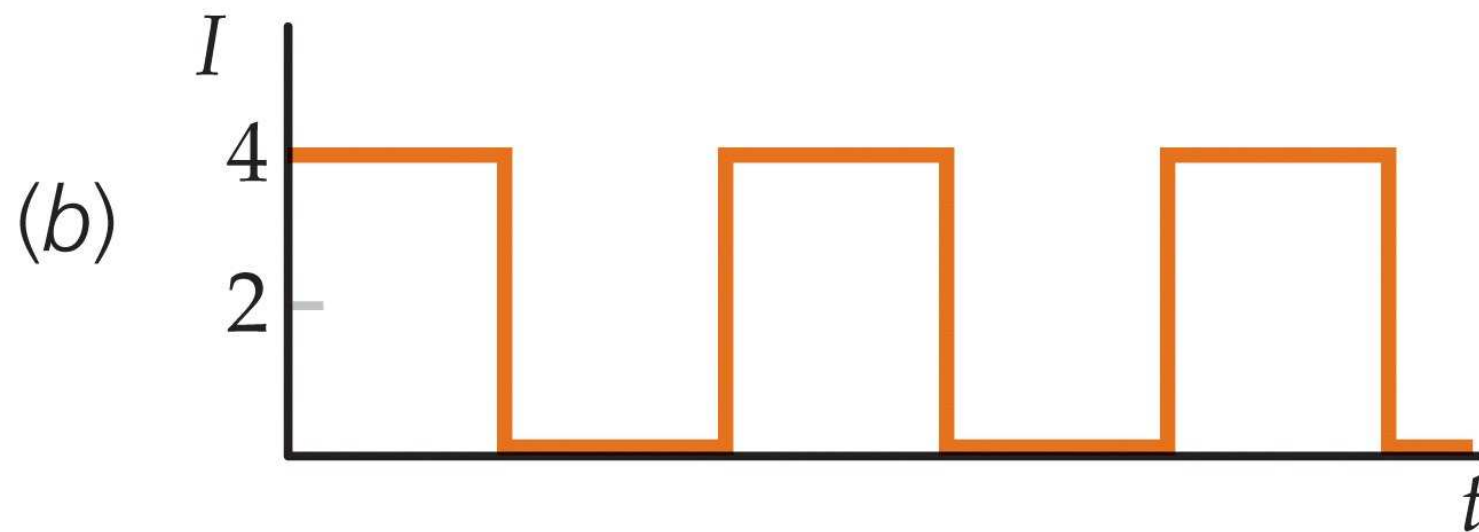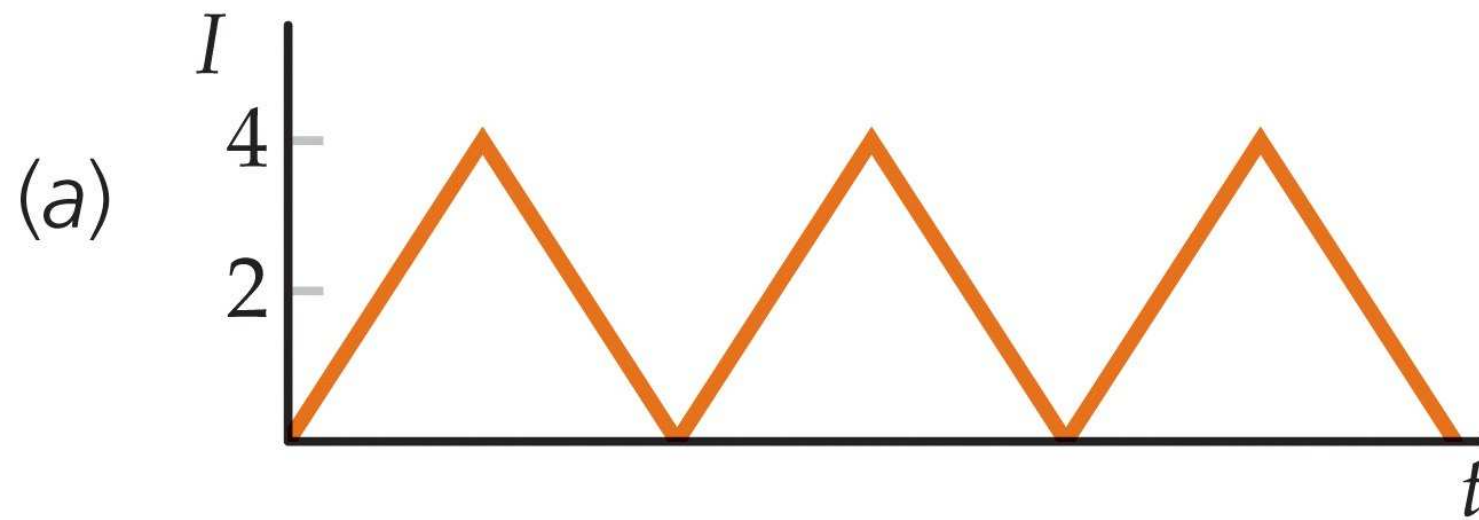



29.119

